



PUNE INSTITUTE OF COMPUTER TECHNOLOGY, PUNE - 411043

Department of Electronics & Telecommunication Engineering

INDEX

Subject: VLSI DEVICES & TECHNOLOGY (404181)

ROLL NO.: 42247 DIV. 6

YEAR: 2021-2022

SEMESTER: 7

List of Laboratory Experiments

S. No.	Title of Experiment	Performance Date	Submission Date	Sign
	<u>PART-A</u> To write VHDL code, simulate with test bench, synthesis, implement on PLD			
A.1	4 bit ALU for add, subtract, AND, NAND, XOR, XNOR, OR, & ALU pass.	14/09/2021	21/09/2021	
A.2	Universal Shift register with mode selection input for SISO, SIPO, PISO, & PIPO modes	21/09/2021	28/09/2021	
A.3	FIFO memory (4 X 8)	05/10/2021	12/10/2021	
A.4	LCD interface	12/10/2021	19/10/2021	
	<u>PART-B</u> To prepare CMOS layout in selected technology, simulate with and without capacitive load, comment on rise, and fall times.			
B.1.a	INVERTER & Analyses	09/11/2021	16/11/2021	
B.1.b	NAND – AND , NOR – OR Logic Gates	09/11/2021	16/11/2021	
B.1.c	TRANSMISSION GATE (TG)	16/11/2021	23/11/2021	
B.2	2:1 MUX Using TG	16/11/2021	23/11/2021	
B.1.d	HALF-ADDER (Using MUX , MUX Using TG)	16/11/2021	23/11/2021	
B.3.a	1-bit SRAM Cell Using NMOS Switch	23/11/2021	30/11/2021	
B.3.b	1-bit SRAM Cell Using TG Switch	23/11/2021	30/11/2021	

This is to certify that Shri/Kum Makarand Milind Pundlik has carried out the above mentioned 11 experiments in VLSI Devices & Technology laboratory of the institute.


For PUNE INSTITUTE OF COMPUTER TECHNOLOGY,
Pune: 43

Date: 16/12/2021
PRINCIPAL

} Staff
In charge

Class	:	BE-6
Roll. No	:	42247
Assignment No.	:	A.1
Assignment Name	:	4-Bit ALU
Date Of Performance	:	18/08/2021

BLOCK DIAGRAM

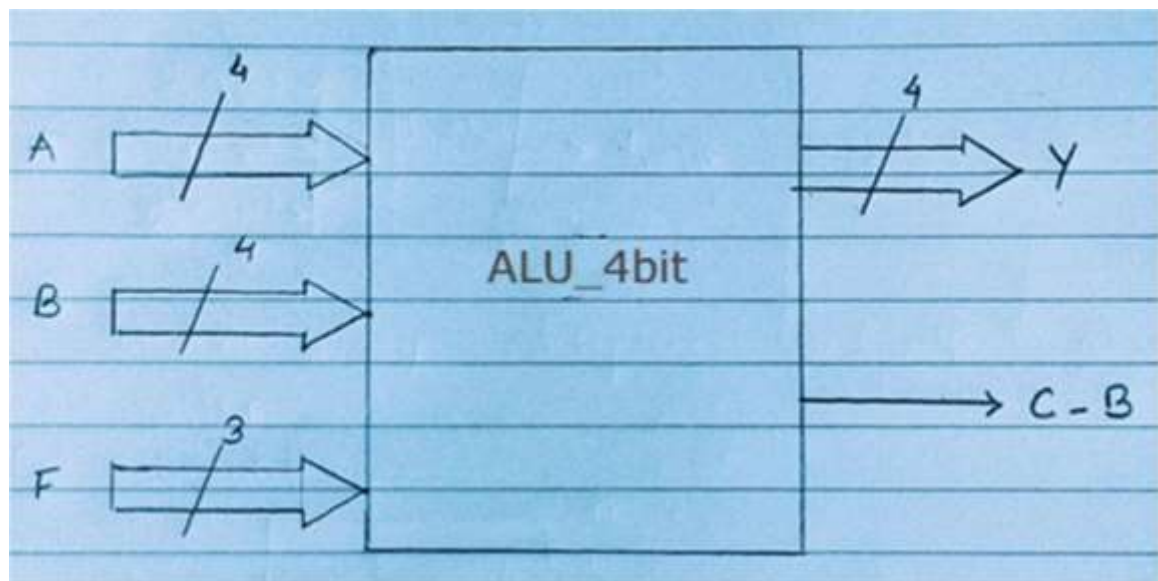

FUNCTION TABLE

F			Y	C_B
F(2)	F(1)	F(0)		
0	0	0	$A.B$	x
0	0	1	$\overline{A.B}$	x
0	1	0	$A+B$	x
0	1	1	$A \oplus B$	x
1	0	0	$\overline{A \odot B}$	x
1	0	1	$\overline{A+B}$	x
1	1	0	$A + B$	CARRY
1	1	1	$A - B$	BORROW

MAIN VHDL MODEL (MVM)

```
library IEEE; use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_UNSIGNED.ALL;
use IEEE.NUMERIC_STD.ALL;
```

entity ALU_4bit is

```
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
      B : in STD_LOGIC_VECTOR (3 downto 0);
      F : in STD_LOGIC_VECTOR (2 downto 0);
      Y : out STD_LOGIC_VECTOR (3 downto 0);
      C_B : out STD_LOGIC
    );
```

end ALU_4bit;

architecture ALU_4bit_arch of ALU_4bit is

```
signal result:STD_LOGIC_VECTOR(4 downto 0):="00000";
```

begin

process(A,B,F)

begin



CASE F IS

when "000" =>

result <= '0' & (A AND B);

when "001" => result <= '0' & (A NAND B);

when "010" => result <= '0' & (A OR B);

when "011" => result <= '0' & (A XOR B);

when "100" => result <= '0' & (A XNOR B);

when "101" => result <= '0' & (A NOR B);

when "110" => result <= ('0' & A)+('0' & B);

when others => if A < B then result <= '0' & (NOT B); result <= result+1;
result <= ('0' & A) + result; result <= (NOT result) + 1;
result <= (NOT(('0' & A) + ('0' & (NOT B)) + 1))+1; else
result <= ('0' & A)-('0' & B);
end if ;


end CASE;

end process;


Y <= result(3 downto 0);


C_B <= result(4);

```
end ALU_4bit_arch;
```



RTL SCHEMATIC:

 

 

SYNTHESIS REPORT

a) Device Utilization Summary:

=====

* Final Report *

Final Results

RTL Top Level Output File Name : ALU_4bit.ngr

Top Level Output File Name : ALU_4bit

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : No

Design Statistics

IOs : 16

Cell Usage :

BELS : 57

LUT1 : 4

LUT3 : 18

LUT4 : 13

MUXCY : 4

MUXF5 : 9

MUXF6 : 4

XORCY : 5

IO Buffers : 16 # IBUF : 11 # OBUF :

===== Device
utilization summary:

Selected Device : 3s250epq208-5

Number of Slices: 19 out of 2448 0%
Number of 4 input LUTs: 35 out of 4896 0%
Number of IOs: 16
Number of bonded IOBs: 16 out of 158 10%

b) TIMING REPORT:

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE. FOR ACCURATE
TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT GENERATED AFTER PLACE-
and-ROUTE.

Clock Information:

No clock signals found in this design Asynchronous Control Signals Information:

No asynchronous control signals found in this design Timing Summary:

Speed Grade: -5

Minimum period: No path found

Minimum input arrival time before clock: No path found

Maximum output required time after clock: No path found

Maximum combinational path delay: 13.714ns

Timing Detail:

All values displayed in nanoseconds (ns)

TESTBENCH VHDL MODEL (TVM)

LIBRARY ieee;



```
USE ieee.std_logic_1164.ALL;
```

```
USE ieee.std_logic_unsigned.ALL;
```

```
ENTITY ALU_4bit_tb IS
```

```
END ALU_4bit_tb;
```

```
ARCHITECTURE behavior OF ALU_4bit_tb IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT ALU_4bit
```

```
PORT(
```

```
A: IN std_logic_vector(3 downto 0);
```

```
B: IN std_logic_vector(3 downto 0);
```

```
    F : IN std_logic_vector(2 downto 0);
```

```
    Y : OUT std_logic_vector(3 downto 0);
```

```
        C_B : OUT std_logic
```

```
);
```

```
END COMPONENT;
```

```
--Inputs
```

```
signal A : std_logic_vector(3 downto 0) := "0010"; signal B : std_logic_vector(3 downto 0) :=  
"1111"; signal F : std_logic_vector(2 downto 0) := (others => '1');
```

```
--Outputs
```

```
signal Y : std_logic_vector(3 downto 0);
```

```
signal C_B : std_logic;
```

```
-- No clocks detected in port list. Replace <clock> below with
```

```
-- appropriate port name
```

```
BEGIN
```

-- Instantiate the Unit Under Test (UUT)

```
    uut: ALU_4bit PORT MAP (  
A=> A,  
B=> B,  
    F=> F,  
    Y=> Y,  
    C_B=> C_B  
    );  
  
-- Stimulus process  stim_proc_F: process  
begin
```


```
F <= F + 1;
```

wait for 25 ns;

end process;

END;

ISIM WAVEFORMS

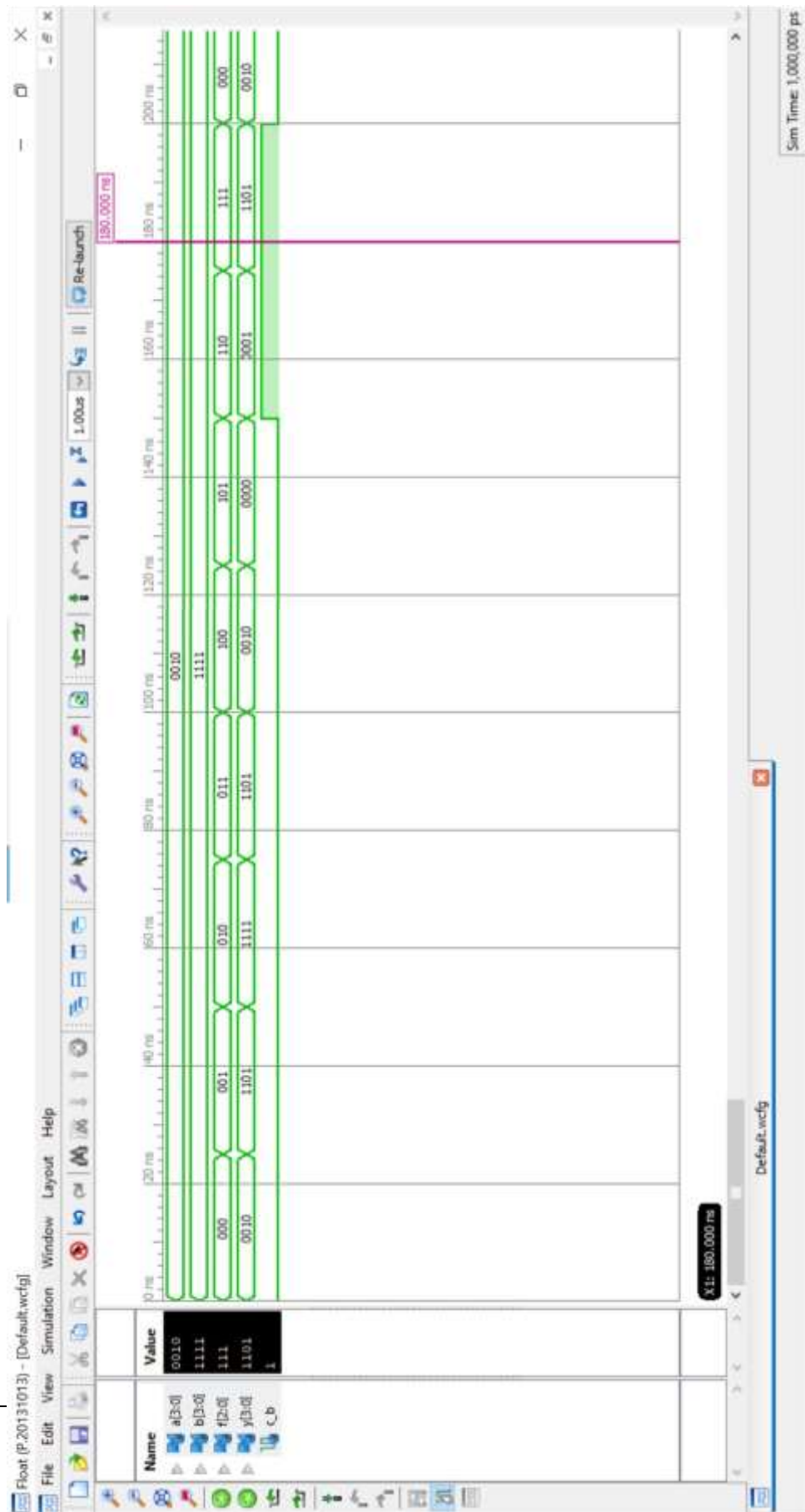

PIN-LOCKING REPORT

PlanAhead Generated physical constraints

NET "A[3]" LOC = P205;

NET "A[2]" LOC = P206;

NET "A[1]" LOC = P203;

NET "A[0]" LOC = P200;

NET "B[3]" LOC = P192;

NET "B[2]" LOC = P193;

NET "B[1]" LOC = P189;

NET "B[0]" LOC = P190;

NET "F[2]" LOC = P179;

NET "F[1]" LOC = P180;

NET "F[0]" LOC = P177;

NET "Y[3]" LOC = P165;

NET "Y[2]" LOC = P167;


NET "Y[1]" LOC = P163;

NET "Y[0]" LOC = P164;

NET "C_B" LOC = P153;

CONCLUSION


Thus, we have:

 

-
- 1) Modeled a 4-Bit ALU using Behavioral Modeling Style.
 - 2) Observed following Schematics: RTL & Technology Schematics generated Post-Synthesis.
 - 3) Interpreted Device Utilization Summary in terms of LUTs, SLICES, IOBs, Multiplexers & D FFs used out of the available device resources.
 - 4) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency, setup time, hold time.
 - 5) Written a TESTBENCH to verify the functionality of 4-Bit ALU & verified the functionality as per the FUNCTION-TABLE, by observing ISIM Waveforms.
 - 6) Used PlanAhead Editor for pin-locking.
 - 7) Prototyped the FPGA XC3S250EPQ208-5 to realize 4-Bit ALU & verified its operation by giving suitable input combinations.

Class	:	BE-6
Roll. No	:	42247
Assignment No.	:	A.2
Assignment Name	:	Universal Shift Register
Date Of Performance	:	08/09/2021

BLOCK DIAGRAM

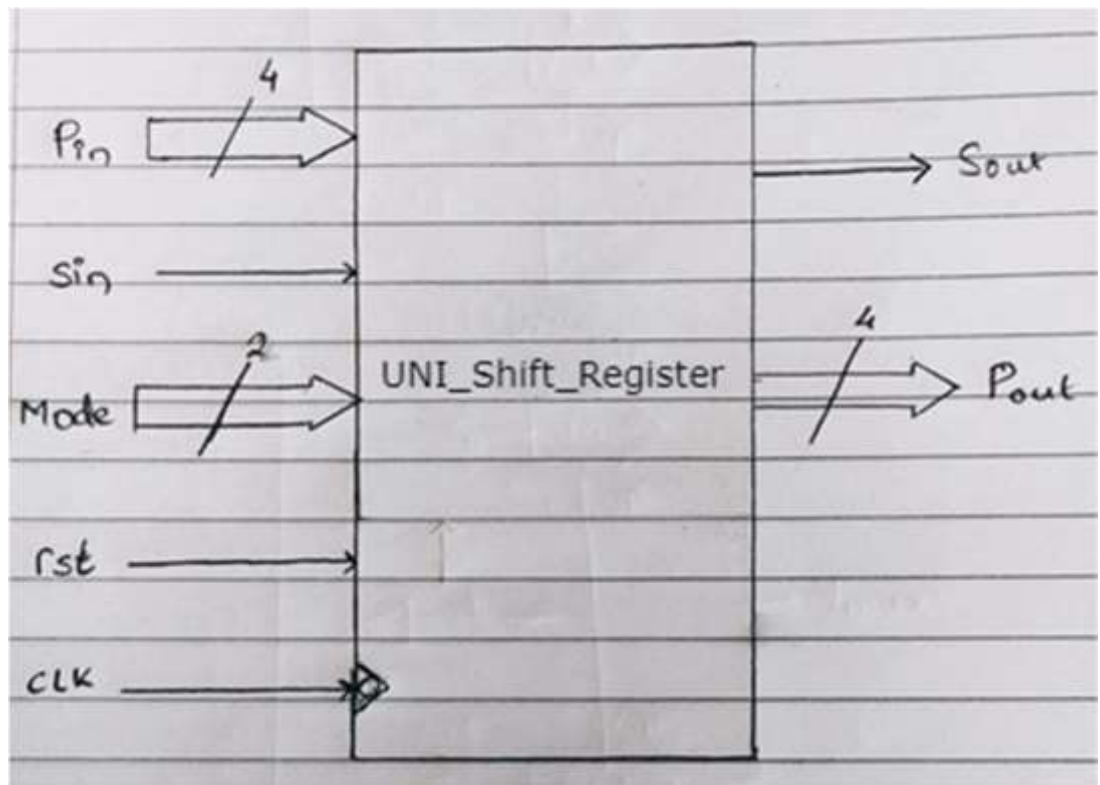

FUNCTION TABLE

rst	clk	mode		Outputs
		mode(1)	mode(0)	
1	x	x	x	Sout = 0 , Pout = "0000"
0	↓	0	0	Serial In Serial Out (SISO)
0	↓	0	1	Serial In Parallel Out (SIPO)
0	↓	1	0	Parallel In Serial Out (PISO)
0	↓	1	1	Parallel In Parallel Out (PIPO)

MAIN VHDL PROGRAM (MVM)

library IEEE;

use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_UNSIGNED.ALL;

use IEEE.NUMERIC_STD.ALL;

entity UNI_Shift_Register is Port (rst : in STD_LOGIC; clk : in STD_LOGIC; Sin : in
STD_LOGIC;

mode : in STD_LOGIC_VECTOR (1 downto 0);

Pin : in STD_LOGIC_VECTOR (3 downto 0);

Sout : out STD_LOGIC;

Pout : out STD_LOGIC_VECTOR (3 downto 0)

);

end UNI_Shift_Register;

architecture UNI_Shift_Register_arch of UNI_Shift_Register is SIGNAL temp : STD_LOGIC_VECTOR (3
downto 0):="0000";

begin



```
PROCESS(rst, clk, mode, Sin, Pin)
BEGIN
    IF rst = '1' THEN
        Pout <= "0000";
        Sout <= '0';

    ELSIF FALLING_EDGE(clk) THEN

        CASE mode IS

            WHEN "00" =>
```

```
temp(3 downto 1) <= temp(2 downto 0);
```

```
temp(0) <= Sin;

Sout <= temp(3);
Pout <= "0000";

WHEN "01" =>
    temp(3 downto 1) <= temp(2 downto 0);
    temp(0) <= Sin;
Pout <= temp;

Sout <= '0';

WHEN "10" =>
    temp <= Pin;
    Sout <= temp(3);
temp(3 downto 1) <= temp(2 downto 0);
Pout <= "0000";


WHEN OTHERS =>
    Pout <= Pin;
    Sout <= '0';

END CASE;

END IF;


END PROCESS;
```

```
end UNI_Shift_Register_arch;
```

 


RTL SCHEMATIC:

UNI_Shift_Register

 


UNI_Shift_Register

UNI_Shift_Register:1

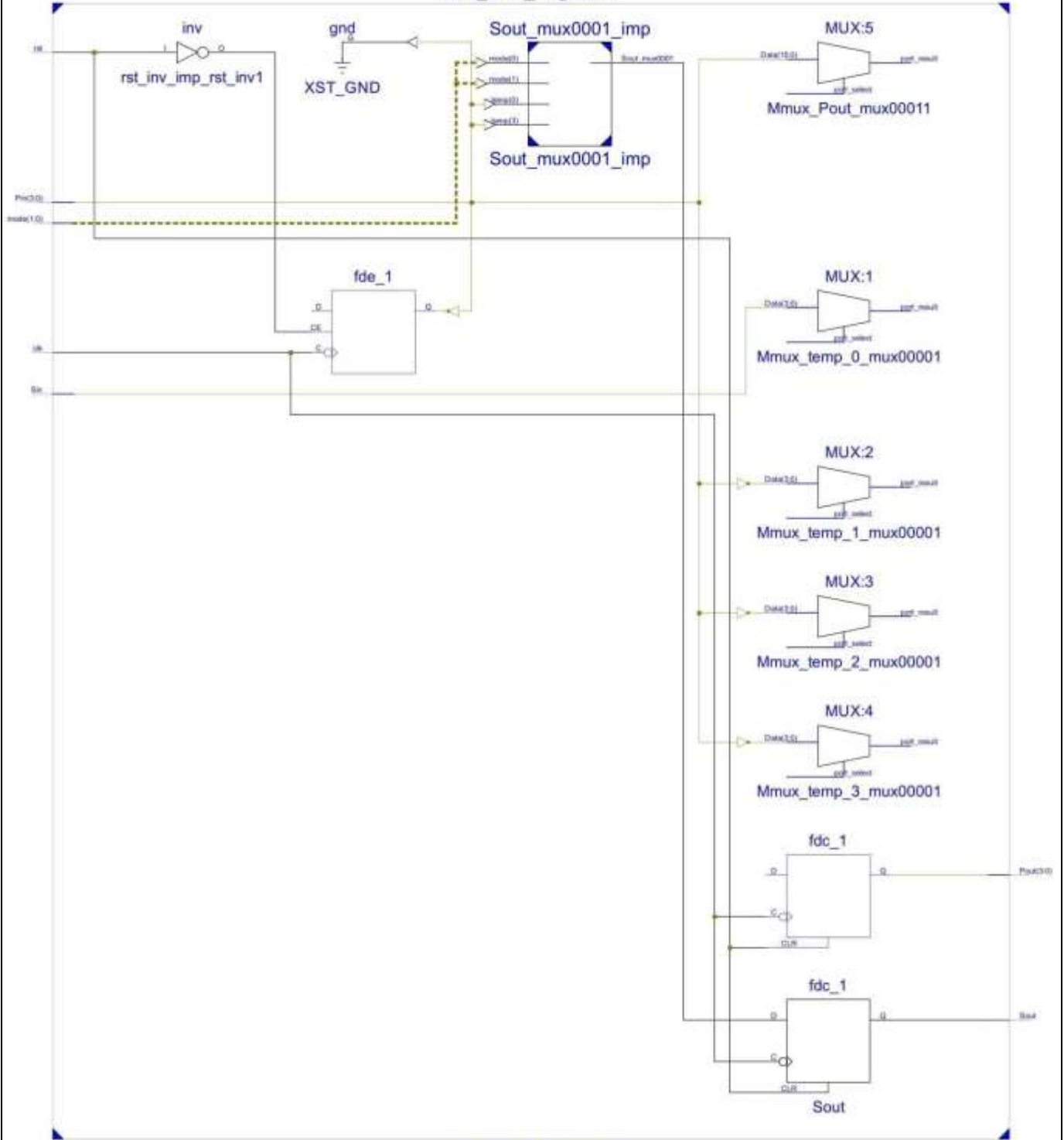

UNI_Shift_Register

TECHNOLOGY SCHEMATIC

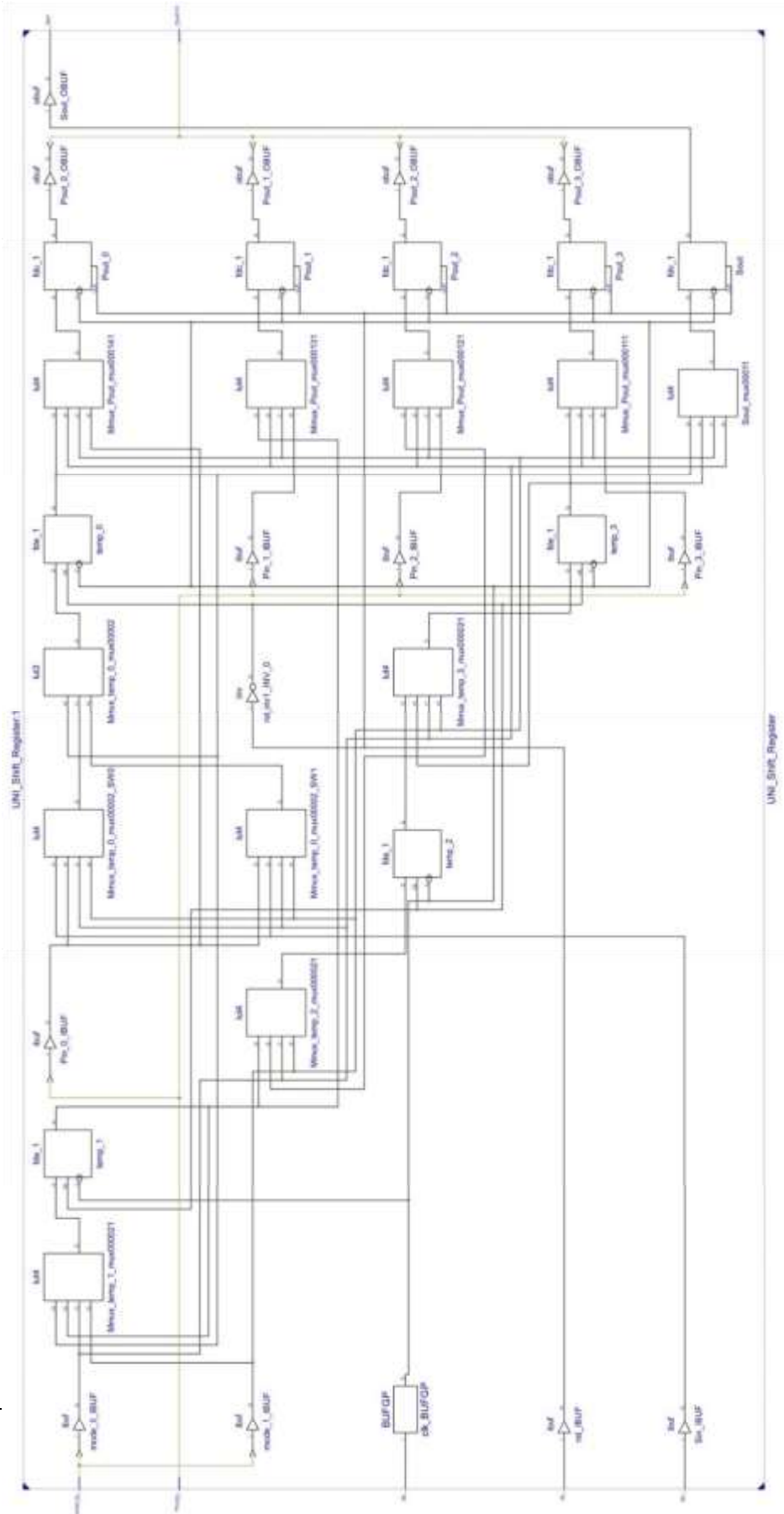

SYNTHESIS REPORT

a) Device Utilization Summary:

=====

* Final Report *

=====

Final Results

RTL Top Level Output File Name : UNI_Shift_Register.ngr

Top Level Output File Name : UNI_Shift_Register

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : No

Design Statistics

IOs : 14

Cell Usage :

BELS : 12

INV : 1

LUT3 : 1

LUT4 : 10

FlipFlops/Latches : 9

FDC_1 : 5

FDE_1 : 4

Clock Buffers : 1

BUFGP : 1

IO Buffers : 13

IBUF : 8

OBUF :5

===== Device

utilization summary:

Selected Device : 3s250epq208-5

Number of Slices:	6 out of 2448	0%	
Number of Slice Flip Flops:	9 out of 4896	0%	
Number of 4 input LUTs:	12 out of 4896	0%	
Number of IOs:	14		
Number of bonded IOBs:	14 out of 24	4%	Number of GCLKs: 1 out of 158 8%

b) TIMING REPORT:

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.

FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

	+	+	+	
Clock Signal		Clock buffer(FF name)		Load
-----+-----+ clk		BUFGP		9
	+	+	+	

Asynchronous Control Signals Information:

	+	+	+	
Control Signal		Buffer(FF name)		Load
---+-----+ rst		IBUF		5
	+	+	+	

Timing Summary:

Speed Grade: -5

Minimum period: 1.923ns (Maximum Frequency: 520.034MHz)

Minimum input arrival time before clock: 4.009ns

Maximum output required time after clock: 4.040ns

Maximum combinational path delay: No path found

Timing Detail:

All values displayed in nanoseconds (ns)

TESTBENCH PROGRAM (TVM)

LIBRARY ieee;

```
USE ieee.std_logic_1164.ALL;
```

```
ENTITY UNI_Shift_Register_tb IS
```

```
END UNI_Shift_Register_tb;
```

```
ARCHITECTURE behavior OF UNI_Shift_Register_tb IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT UNI_Shift_Register
```

```
PORT(    rst : IN std_logic;    clk : IN std_logic;
```

```
    mode : IN std_logic_vector(1 downto 0);
```

```
    Sin : IN std_logic;
```

```
    Pin : IN std_logic_vector(3 downto 0);
```

```
    Sout : OUT std_logic;
```

```
    Pout : OUT std_logic_vector(3 downto 0)
```

```
);
```

```
END COMPONENT;
```

```
--Inputs  signal rst : std_logic := '0';  signal clk : std_logic := '1';
```

```
signal mode : std_logic_vector(1 downto 0) := (others => '0');
```

```
signal Sin : std_logic := '0';
```

```
signal Pin : std_logic_vector(3 downto 0) := "1010";
```

```
--Outputs
```

```
signal Sout : std_logic;
```

```
signal Pout : std_logic_vector(3 downto 0);
```

```
-- Clock period definitions  constant clk_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)  uut: UNI_Shift_Register PORT MAP (
```

rst => rst, clk => clk,

mode => mode,

Sin => Sin,

Pin => Pin,

Sout => Sout,

Pout => Pout

);



```
-- Clock process definitions  clk_process :process  begin
```

```
    clk<=NOT(clk);
```

```
    wait for clk_period/2 ;
```

```
end process;
```

```
-- Stimulus process  stim_proc_mode: process  begin          mode<="00";
```

```
    wait for 80 ns;
```

```
    mode<="01";
```

```
    wait for 50 ns;
```

```
    mode<="10";
```

```
    wait for 50 ns;
```

```
    mode<="11";
```

```
    wait for 20 ns;  end process;
```

```
stim_proc_Sin:process
```

```
    begin
```

```
    wait for 10 ns;
```

```
    Sin<='1';      wait for 10 ns;
```

```
    Sin<='0';      wait for 10 ns;
```

```
    Sin<='1';      wait for 10 ns;
```

```
    Sin<='0';      wait for 10 ns;
```

Sin<= '0'; wait for 40 ns;

```
Sin<='1';      wait for 10 ns;
```

```
        Sin<='0';        wait for 10 ns;

        Sin<='1';        wait for 10 ns;

        Sin<='0';        wait for 10 ns;


Sin<= '0';        wait ;

        end process;

stim_proc_rst:process  begin
rst<='0';
wait for 300 ns;

rst<='1';        wait for 10 ns;  end process;
END;
```

ISIM WAVEFORMS

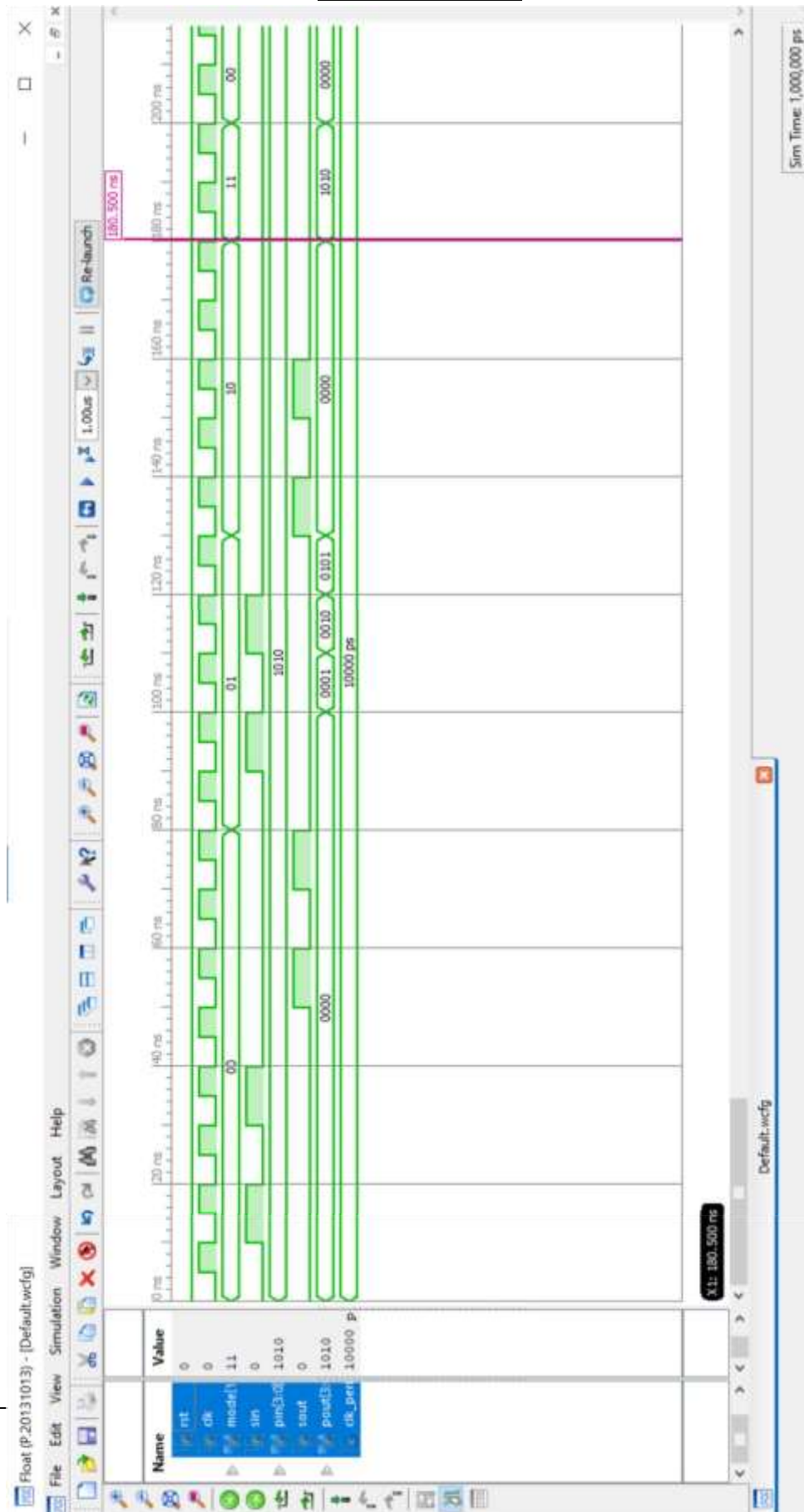

PIN-LOCKING REPORT

PlanAhead Generated physical constraints

NET "clk" LOC = P132;

NET "rst" LOC = P204;

NET "mode[1]" LOC = P205;

NET "mode[0]" LOC = P206;

NET "Sin" LOC = P203;

NET "Pin[3]" LOC = P202; NET "Pin[2]" LOC = P197;

NET "Pin[1]" LOC = P199;

NET "Pin[0]" LOC = P196;

NET "Sout" LOC = P193;

NET "Pout[3]" LOC = P186;


NET "Pout[2]" LOC = P187;

NET "Pout[1]" LOC = P185;

NET "Pout[0]" LOC = P181;

CONCLUSION


Thus, we have:

 

-
- 8) Modeled a Universal Shift Register using Behavioral Modeling Style.
 - 9) Observed following Schematics: RTL & Technology Schematics generated Post-Synthesis.
 - 10) Interpreted Device Utilization Summary in terms of LUTs, SLICES, IOBs, Multiplexers & D FFs used out of the available device resources.
 - 11) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency.
 - 12) Written a TESTBENCH to verify the functionality of Universal Shift Register & verified the functionality as per the FUNCTION-TABLE, by observing ISIM Waveforms.
 - 13) Used PlanAhead Editor for pin-locking.
 - 14) Prototyped the FPGA XC3S250EPQ208-5 to realize Universal Shift Register & verified its operation by giving suitable input combinations.

Class	:	BE-6
Roll. No	:	42247
Assignment No.	:	A.4
Assignment Name	:	FPGA-LCD Interfacing
Date Of Performance	:	22/09/2021

BLOCK DIAGRAM

 

FUNCTION TABLE

rst	clk	lcd_data	lcd_rs	lcd_en
1	x	38h	0	x
0	↑	06h	0	↑
0	↑	0Ch	0	↑
0	↑	01h	0	↑
0	↑	50h (P)	1	↑
0	↑	49h (I)	1	↑
0	↑	43h (C)	1	↑
0	↑	54h (T)	1	↑
0	↑	20h ()	1	↑

MAIN VHDL PROGRAM: (MVM)

library IEEE; use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL; use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity LCD_FSM is

```

    Port ( rst : in std_logic;           -- reset
          clk_12Mhz : in std_logic;      -- high freq.
                                              clock
          lcd_rs : out std_logic;         -- LCD RS control
          lcd_en : out std_logic;         -- LCD Enable
          lcd_data : out std_logic_vector(7 downto 0)); -- LCD Data port end LCD_FSM;
```

architecture Behavioral of LCD_FSM is

```

signal div : std_logic_vector(15 downto 0); --- delay timer 1
signal clk_fsm,lcd_rs_s: std_logic; -- LCD
controller FSM states
type state is (reset,func,mode,cur,clear,d0,d1,d2,d3,d4,hold);
signal ps1,nx : state;
```

```
signal dataout_s : std_logic_vector(7 downto 0); --- internal data command multiplexer
```

begin



```
----- clk divider ----- process(rst,clk_12Mhz) begin if(rst = '1')then
```

```
    div <= (others=>'0');
```

```
elseif( clk_12Mhz'event and clk_12Mhz = '1')then
```

```
    div <= div + 1;  end if;
```

```
end process;
```

```
----- clk_fsm <= div(15);
```

```
----- Presetn state Register ----- process(rst,clk_fsm) begin if(rst = '1')then
```

```
    ps1    <= reset;
```

```
elseif (rising_edge(clk_fsm)) then
```

```
    ps1    <= nx;
```

```
end if; end process; ----- state and output decoding process process(ps1) begin
```

```
case(ps1) is
```

when reset =>

```

        nx      <= func;
        lcd_rs_s    <= '0';
        dataout_s    <= "00111000";        -- 38h

when func    =>
        nx      <= mode;
        lcd_rs_s    <= '0';
        dataout_s    <= "00111000";        -- 38h

when mode    =>
        nx      <= cur;
        lcd_rs_s    <= '0';
        dataout_s    <= "00000110";        -- 06h

when cur      =>
        nx      <= clear;
        lcd_rs_s    <= '0';
        dataout_s    <= "00001100";        -- 0Ch  curser at starting point of
line1
when clear=>
        nx      <= d0;
        lcd_rs_s    <= '0';
        dataout_s    <= "00000001";        -- 01h

when d0      =>
        lcd_rs_s    <= '1';
        dataout_s    <= "01010000";        -- P ( Decimal = 80 , HEX =
50 )
        nx      <= d1;

when d1      =>
        lcd_rs_s    <= '1';
        dataout_s    <= "01001001";        -- I ( Decimal = 73 , HEX = 49
)
        nx      <= d2;

when d2      =>
        lcd_rs_s    <= '1';
        dataout_s    <= "01000011";        -- C ( Decimal = 67 , HEX =
43 )
        nx      <= d3;

```

```
when d3      =>
    lcd_rs_s      <= '1';
    dataout_s      <= "01010100";      -- T ( Decimal = 84 , HEX = 54
    )
    nx      <= d4;

when d4      =>
    lcd_rs_s      <= '1';
    dataout_s <= "00100000";      -- space ( Decimal = 32 , HEX = 20 )
    nx      <= hold;

when hold    =>
    lcd_rs_s      <= '0';
    dataout_s <= "00000000";      -- hold ( Decimal = 32 , HEX = 00 ) ,
NULL
    nx      <= hold;


when others=>
    nx      <= reset;
    lcd_rs_s      <= '0';
    dataout_s <= "00000001"; -- CLEAR ( Decimal = 1 , HEX = 01 )

end case; end process;


lcd_en <= clk_fsm; lcd_rs <= lcd_rs_s;


lcd_data <= dataout_s;
```

end Behavioral;

 


RTL SCHEMATIC:

 

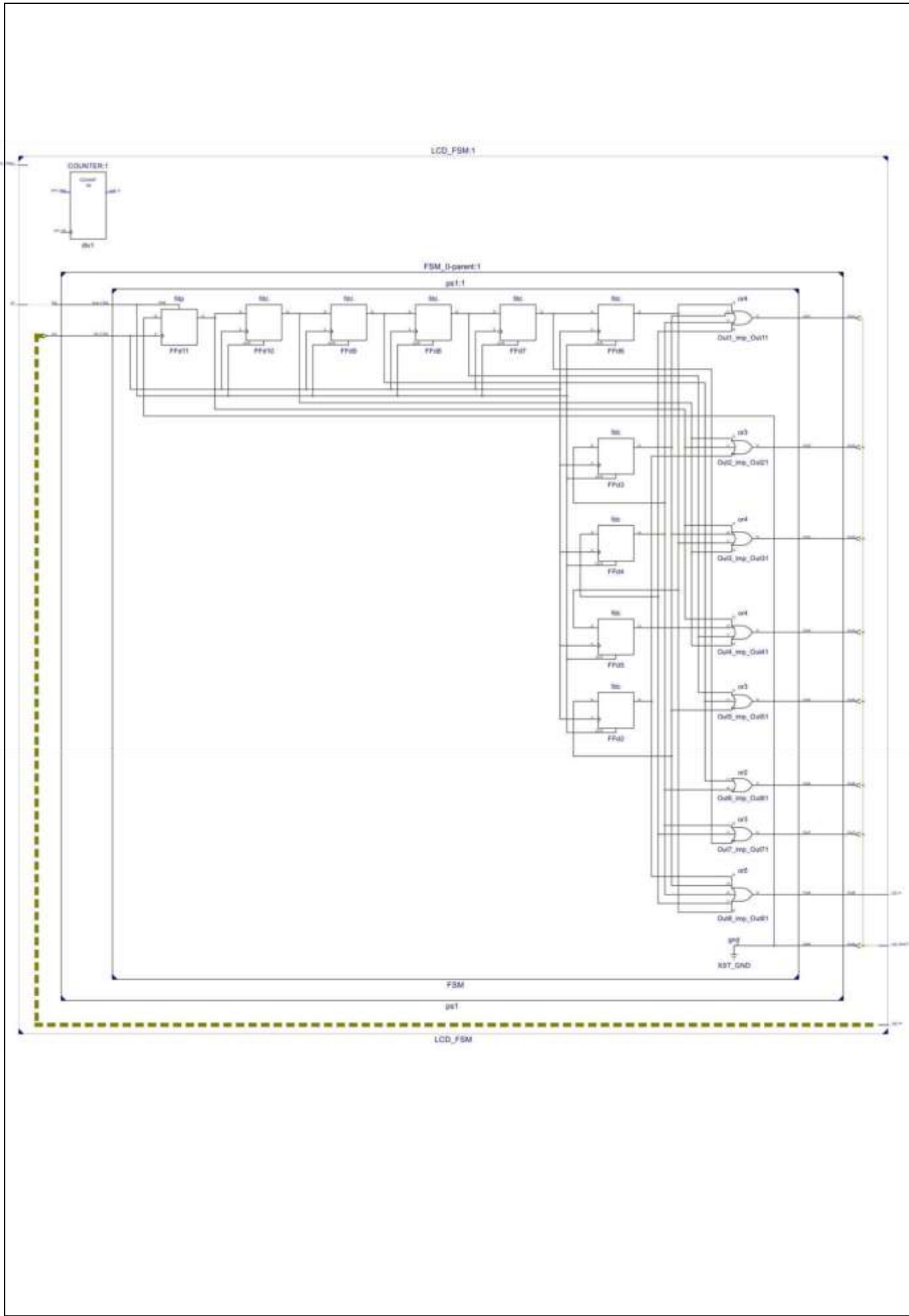

TECHNOLOGY SCHEMATIC

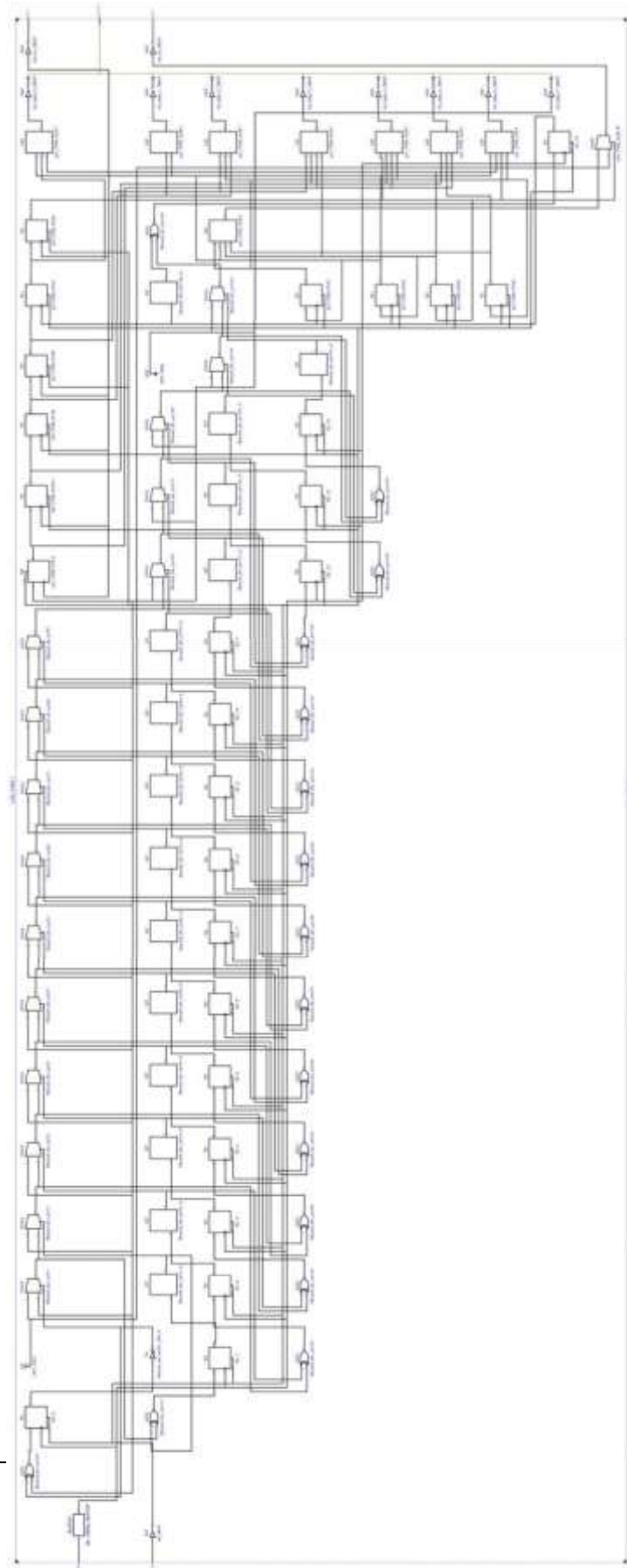

SYNTHESIS REPORT

a) Device Utilization Summary:

=====

* Final Report *

=====

Final Results

RTL Top Level Output File Name : LCD_FSM.ngr

Top Level Output File Name : LCD_FSM

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : No

Design Statistics

IOs : 12

Cell Usage :

BELS : 58

GND : 1

INV : 1

LUT1 : 15

LUT2 : 1

LUT3 : 3 # LUT4 : 4

MUXCY : 15

MUXF5 : 1

VCC : 1

#	XORCY	:	16
#	FlipFlops/Latches	:	26
#	FDC	:	25
#	FDP	:	1
#	Clock Buffers	:	1
#	BUFGP	:	1
#	IO Buffers	:	11
#	IBUF	:	1
#	OBUF	:	10

=====

Device utilization summary:

Selected Device : 3s250epq208-5

Number of Slices:	15 out of 2448	0%		
Number of Slice Flip Flops:	26 out of 4896	0%		
Number of 4 input LUTs:	24 out of 4896	0%		
Number of IOs:	12			
Number of bonded IOBs:	12 out of 158	7%	Number of GCLKs:	1 out of 24 4%

b) TIMING REPORT:

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.

FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

-----+-----+-----+

Clock Signal	Clock buffer(FF name)	Load	-----+-----
-----+-----+ clk_12Mhz	BUFGP	16	div_15
NONE(ps1_FSM_FFd11)	10		

-----+-----+-----+

INFO:Xst:2169 - HDL ADVISOR - Some clock signals were not automatically buffered by XST with

BUFG/BUFR resources. Please use the buffer_type constraint in order to insert these buffers to the clock signals to help prevent skew problems.

Asynchronous Control Signals Information:

-----+-----+-----+			
Control Signal	Buffer(FF name)	Load	-----+-----
---+-----+ rst	IBUF	26	
-----+-----+-----+			

Timing Summary:

Speed Grade: -5

Minimum period: 3.676ns (Maximum Frequency: 272.072MHz)

Minimum input arrival time before clock: No path found

Maximum output required time after clock: 5.537ns

Maximum combinational path delay: No path found

Timing Detail:

All values displayed in nanoseconds (ns)

TESTBENCH PROGRAM (TVM)

LIBRARY ieee;

USE ieee.std_logic_1164.ALL;

ENTITY LCD_Test IS

END LCD_Test;

ARCHITECTURE behavior OF LCD_Test IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT LCD_FSM

PORT(
rst : IN std_logic; clk_12Mhz : IN std_logic; lcd_rs : OUT std_logic;
lcd_en : OUT std_logic;

lcd_data : OUT std_logic_vector(7 downto 0)

);



```
END COMPONENT;
```

```
--Inputs  signal rst : std_logic := '0';
```

```
signal clk_12Mhz : std_logic := '0';
```

```
--Outputs
```

```
signal lcd_rs : std_logic;  signal lcd_en : std_logic;
```

```
signal lcd_data : std_logic_vector(7 downto 0);
```

```
-- Clock period definitions
```

```
constant clk_12Mhz_period : time := 10 ns;
```

```
BEGIN
```

```
-- Instantiate the Unit Under Test (UUT)
```

```
uut: LCD_FSM PORT MAP (
```

```
    rst => rst,
```

```
    clk_12Mhz => clk_12Mhz,    lcd_rs => lcd_rs,    lcd_en => lcd_en,
```

```
    lcd_data => lcd_data
```

```
);
```

```
-- Clock process definitions  clk_12Mhz_process :process
```

```
begin
```

```
    clk_12Mhz <= '0';          wait for clk_12Mhz_period/2;          clk_12Mhz  
<= '1';
```

```
    wait for clk_12Mhz_period/2;
```

```
end process;
```

```
-- Stimulus process  stim_proc: process
```

```
begin
```

```
    rst <= '1';
```

wait for 20 ns;

rst <= '0';


-- insert stimulus here

```
wait;  
end process;
```

END;



ISIM WAVEFORMS

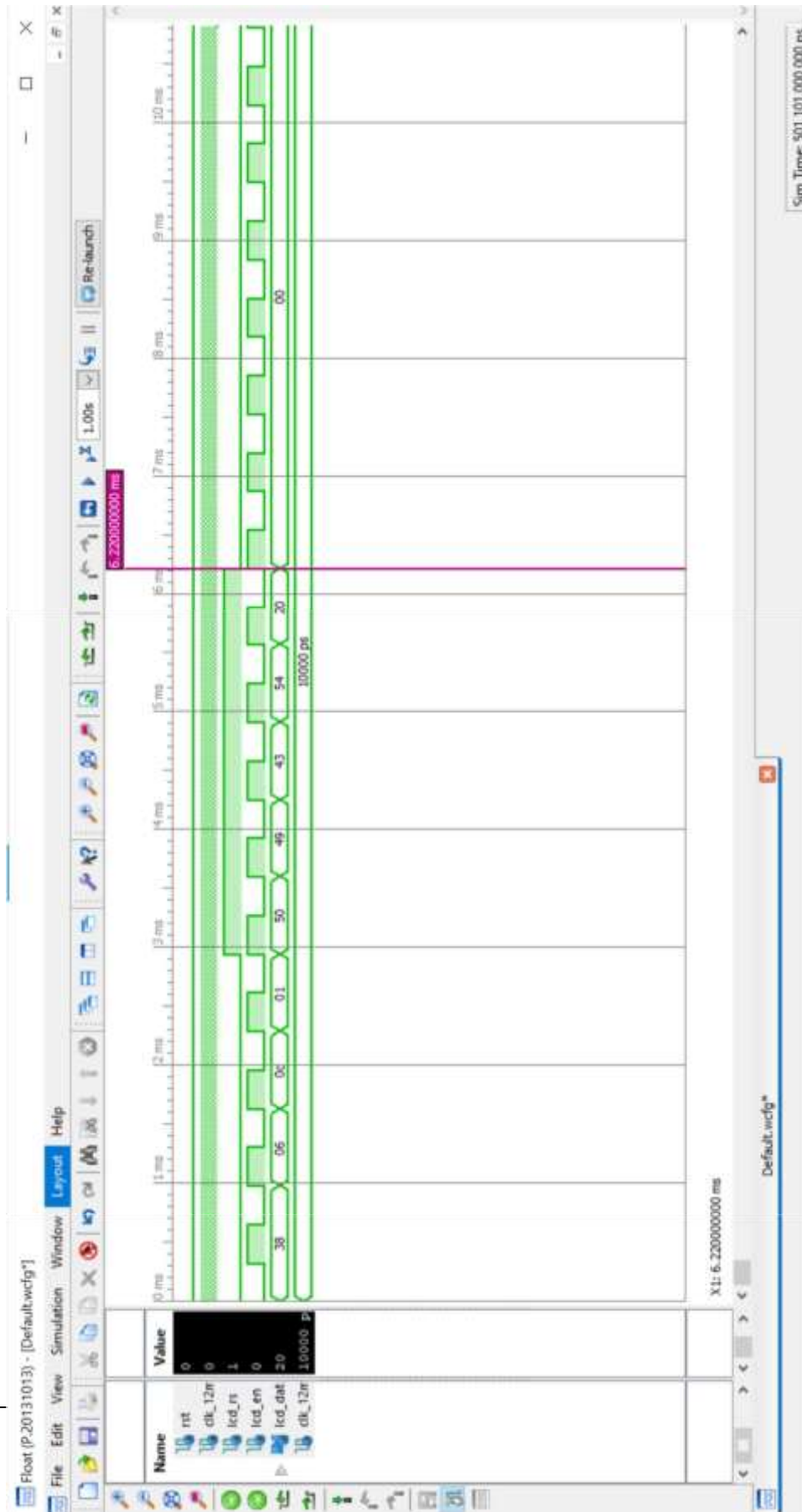

PIN-LOCKING REPORT

PlanAhead Generated physical constraints

NET "clk_12Mhz" LOC = P80;

NET "rst" LOC = P204;

NET "lcd_rs" LOC = P48;

NET "lcd_en" LOC = P49;

NET "lcd_data[0]" LOC = P47;

NET "lcd_data[1]" LOC = P41;

NET "lcd_data[2]" LOC = P39;

NET "lcd_data[3]" LOC = P35;

NET "lcd_data[4]" LOC = P33;


NET "lcd_data[5]" LOC = P31;

NET "lcd_data[6]" LOC = P29;

NET "lcd_data[7]" LOC = P24;

CONCLUSION


Thus, we have:

 

-
- 15) Modeled a FPGA-LCD Interfacing using Behavioral Modeling Style.
 - 16) Observed following Schematics: RTL & Technology Schematics generated Post-Synthesis.
 - 17) Interpreted Device Utilization Summary in terms of LUTs, SLICES, IOBs, Multiplexers & D FFs used out of the available device resources.
 - 18) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency.
 - 19) Written a TESTBENCH to verify the functionality of FPGA-LCD Interfacing & verified the functionality as per the FUNCTION-TABLE, by observing ISIM Waveforms.
 - 20) Used PlanAhead Editor for pin-locking.
 - 21) Prototyped the FPGA XC3S250EPQ208-5 to realize FPGA-LCD Interfacing & verified its operation by giving suitable input combinations.

Class	:	BE-6
Roll. No	:	42247
Assignment No.	:	A.3
Assignment Name	:	FIFO
Date Of Performance	:	15/09/2021

BLOCK DIAGRAM

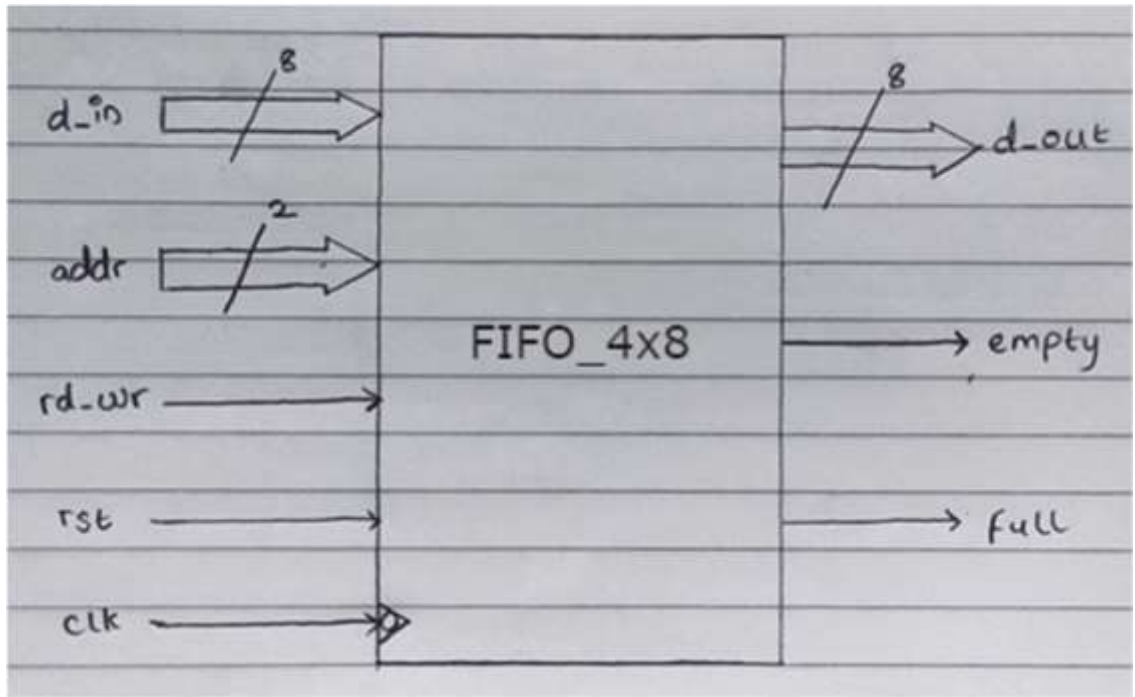

FUNCTION TABLE

rst	clk	addr		rd_wr	d_out	empty	full
		addr(1)	addr(0)				
1	x	x	x	x	(00) ₁₆	1	0
0	↓	0	0	0	mem ₀	0	1
0	↓	0	1	0	mem ₁	0	1
0	↓	1	0	0	mem ₂	0	1
0	↓	1	1	0	mem ₃	0	1
0	↓	0	0	1	mem ₀	0	0
0	↓	0	1	1	mem ₁	0	0
0	↓	1	0	1	mem ₂	0	0
0	↓	1	1	1	mem ₃	0	1

MAIN VHDL PROGRAM (MVM)

library IEEE; use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity FIFO_4x8 is Port (rst : in STD_LOGIC;

clk : in STD_LOGIC;

addr : in STD_LOGIC_VECTOR (1 downto 0) := "00"; d_in : in STD_LOGIC_VECTOR (7
downto 0);

rd_wr : in STD_LOGIC; d_out : out STD_LOGIC_VECTOR (7 downto 0) := "00000000";

empty : out STD_LOGIC := '1'; full : out STD_LOGIC := '0'); end FIFO_4x8;

architecture FIFO_4x8_arch of FIFO_4x8 is

```
TYPE mem IS ARRAY(3 DOWNT0 0) OF STD_LOGIC_VECTOR (7 DOWNT0 0);
```

SIGNAL memory : mem := (others=>(others=>'0'));

begin



```
PROCESS(rst, clk, addr, d_in, rd_wr)
```

```
begin
```

```
    if rst = '1' then
```

```
        d_out <= "00000000";
```

```
        empty <= '1';
```

```
        full <= '0';
```

```
        memory <= (others=>(others=>'0'));
```

```
    elsif falling_edge(clk) then
```

```
        case rd_wr is
```

```
            when '0' =>
```

```
                d_out <= memory(conv_integer(addr));
```

```
                empty <= '0';
```

```
                full <= '1';
```

```
            when others =>
```

```
                memory(conv_integer(addr)) <= d_in;
```

```
                empty <= '0';
```

```
        if addr = "11" then
```

```
            full <= '1';
```

```
        else
```


```
            full <= '0';
```

```
        end if;    end case;
```


```
    end if;
```

```
end process;
```

```
end FIFO_4x8_arch;
```

 

RTL SCHEMATIC:

 

FIFO_4x8

addr(1:0)

d_out(7:0)

d_in(7:0)

clk


empty

rd_wr


rst

full

FIFO_4x8

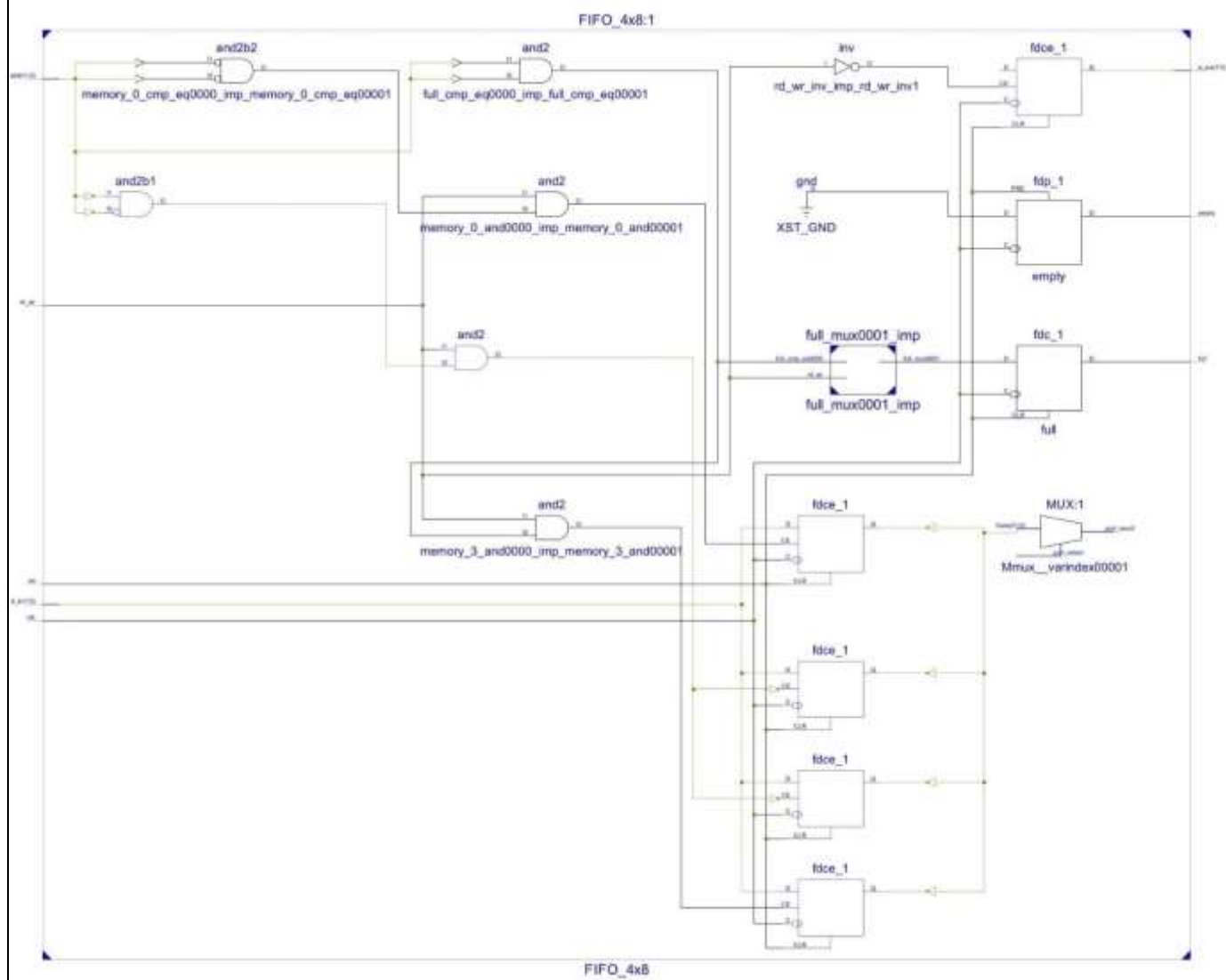

TECHNOLOGY SCHEMATIC

 

SYNTHESIS REPORT

a) Device Utilization Summary:

=====

* Final Report *

=====

Final Results

RTL Top Level Output File Name : FIFO_4x8.ngr

Top Level Output File Name : FIFO_4x8

Output Format : NGC

Optimization Goal : Speed

Keep Hierarchy : No

Design Statistics

IOs : 23

Cell Usage :

BELS : 32

GND : 1

INV : 2

LUT3 : 21

MUXF5 : 8

FlipFlops/Latches : 42

FDC_1 : 1

FDCE_1 : 40

FDP_1 : 1

# Clock Buffers	: 1
# BUFGP	: 1
# IO Buffers	: 22
# IBUF	: 12
# OBUF	: 10

=====

Device utilization summary:

Selected Device : 3s250epq208-5

Number of Slices:	26 out of 2448	1%
Number of Slice Flip Flops:	40 out of 4896	0%
Number of 4 input LUTs:	23 out of 4896	0%
Number of IOs:	23	
Number of bonded IOBs:	23 out of 158	14%
IOB Flip Flops:	2	
Number of GCLKs:	1 out of 24	4%

b) TIMING REPORT:

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.

FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

-----+-----+-----+			
Clock Signal	Clock buffer(FF name)	Load	-----+-----
----+-----+ clk	BUFGP	42	
-----+-----+-----+			

Asynchronous Control Signals Information:

-----+-----+-----+

Control Signal	Buffer(FF name)	Load	-----+-----
---+-----+ rst_inv(rst_inv1_INV_0:O)	NONE(d_out_0)	42	
-----+-----+-----+			

Timing Summary:

Speed Grade: -5


Minimum period: 2.098ns (Maximum Frequency: 476.644MHz)

Minimum input arrival time before clock: 3.955ns

Maximum output required time after clock: 4.040ns

Maximum combinational path delay: No path found

Timing Detail:

 

All values displayed in nanoseconds (ns)

TESTBENCH PROGRAM (TVM)

LIBRARY ieee; USE ieee.std_logic_1164.ALL; use ieee.numeric_std.ALL;

ENTITY FIFO_4x8_tb IS

END FIFO_4x8_tb;

ARCHITECTURE behavior OF FIFO_4x8_tb IS

-- Component Declaration for the Unit Under Test (UUT)

COMPONENT FIFO_4x8

PORT(
 rst : IN std_logic; clk : IN std_logic;
 addr : IN std_logic_vector(1 downto 0); d_in : IN std_logic_vector(7 downto 0);
rd_wr : IN std_logic;
 d_out : OUT std_logic_vector(7 downto 0);
 empty : OUT std_logic;

full : OUT std_logic

);



END COMPONENT;

--Inputs signal rst : std_logic := '0'; signal clk : std_logic := '1';

```
signal addr : std_logic_vector(1 downto 0) := (others => '0');  signal d_in : std_logic_vector(7
```

```
downto 0) := (others => '0');

signal rd_wr : std_logic := '0';

--Outputs

signal d_out : std_logic_vector(7 downto 0);

signal empty : std_logic;

signal full : std_logic;

-- Clock period definitions

constant clk_period : time := 10 ns;

BEGIN

-- Instantiate the Unit Under Test (UUT)

 uut: FIFO_4x8 PORT MAP (
    rst => rst,      clk => clk,      addr => addr,      d_in => d_in,      rd_wr => rd_wr,
    d_out => d_out,
    empty => empty,
    full => full
  );

-- Clock process definitions  clk_process :process
begin

    clk <= not(clk);

wait for clk_period/2;  end process;

-- Stimulus process  stim_proc: process
begin

    rst <= '0';

    wait for clk_period;
```

```
rst <= '1'; wait for clk_period;
```

```
rd_wr <= '1';
```

```
for address in 0 to 3 loop  
std_logic_vector(to_unsigned(address, 2));
```

```
addr <=
```

```
d_in <= std_logic_vector(to_unsigned(63*(address + 1), 8));
```


```
wait for clk_period*2;
    end loop;

    d_in <= std_logic_vector(to_unsigned(0, 8));

    rd_wr <= '0';
    for address in 0 to 3 loop
        addr <= std_logic_vector(to_unsigned(address, 2));
    wait for clk_period*2;    end loop;
    end process;

END;
```

ISIM WAVEFORMS

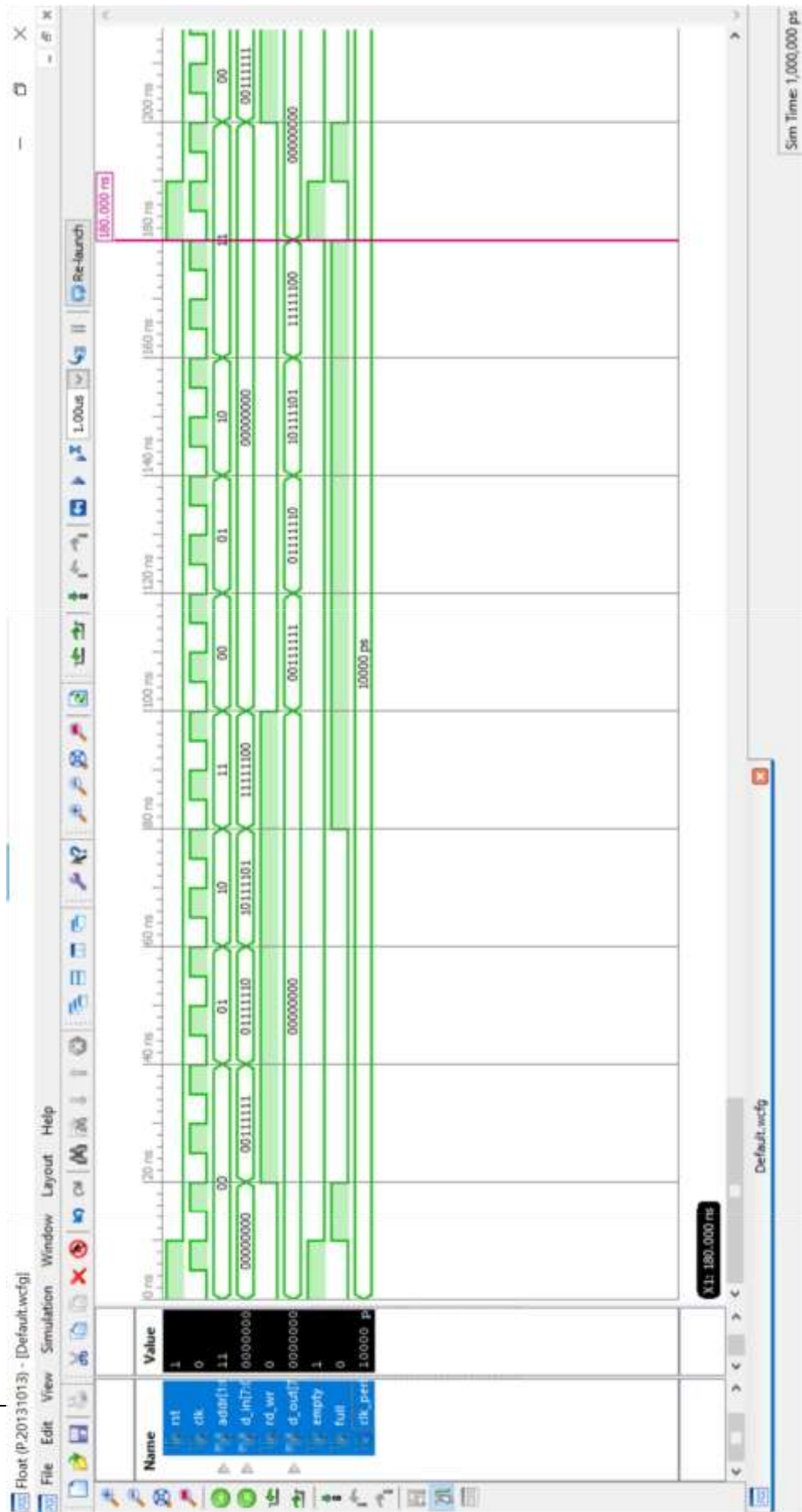

PIN-LOCKING REPORT

PlanAhead Generated physical constraints

```
NET "d_in[7]" LOC = P165;    #sw4-0
NET "d_in[6]" LOC = P167;    #sw4-1
NET "d_in[5]" LOC = P163;    #sw4-2
NET "d_in[4]" LOC = P164;
NET "d_in[3]" LOC = P161;
NET "d_in[2]" LOC = P162;
NET "d_in[1]" LOC = P160;
NET "d_in[0]" LOC = P153;    #sw4-7
NET "d_out[7]" LOC = P179;    #sw3-0
NET "d_out[6]" LOC = P180;    #sw3-1
NET "d_out[5]" LOC = P177;
NET "d_out[4]" LOC = P178;
NET "d_out[3]" LOC = P152;
NET "d_out[2]" LOC = P168;
NET "d_out[1]" LOC = P171;
NET "d_out[0]" LOC = P172;    #sw3-7
NET "clk" LOC = P132;
NET "rst" LOC = P204;        #k0
NET "rd_wr" LOC = P184;      #sw2-6
NET "empty" LOC = P199;#sw1-6
```

NET "full" LOC = P196; #sw1-7


CONCLUSION

Thus, we have:


- 22) Modeled a 4x8 FIFO using Behavioral Modeling Style.
 - 23) Observed following Schematics: RTL & Technology Schematics generated Post-Synthesis.
 - 24) Interpreted Device Utilization Summary in terms of LUTs, SLICES, IOBs, Multiplexers & D FFs used out of the available device resources.
 - 25) Interpreted the TIMING Report in terms of Maximum combinational delay as indicative of the Maximum Operating Frequency.
 - 26) Written a TESTBENCH to verify the functionality of 4x8 FIFO & verified the functionality as per the FUNCTION-TABLE, by observing ISIM Waveforms.
 - 27) Used PlanAhead Editor for pin-locking.
 - 28) Prototyped the FPGA XC3S250EPQ208-5 to realize 4x8 FIFO & verified its operation by giving suitable input combinations.
-

Class	BE-6
Roll Number	42247
Assignment Number	B.1.a
Assignment Name	CMOS Inverter
Date of performance	29/09/2021

Block Diagram:-

 


MOSFET-LEVEL SCHEMATIC :

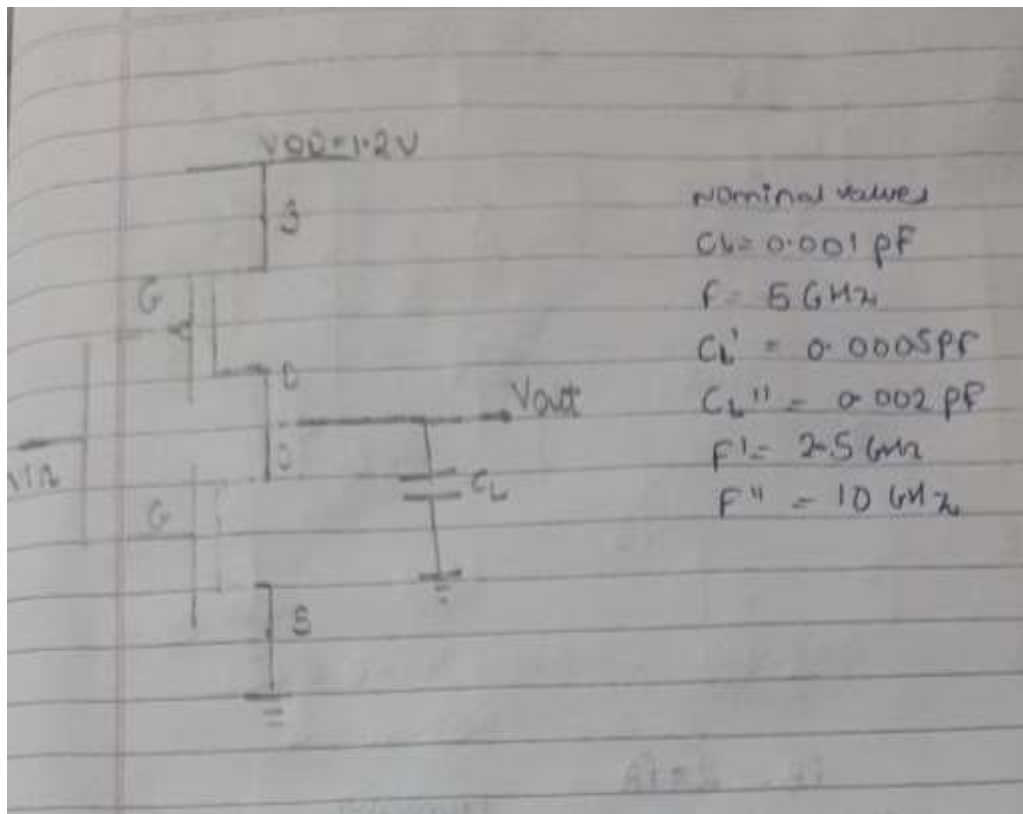

Truth Table:-


V _{in}	V _{out}
0	Strong-1
1	Strong-0

Layout:

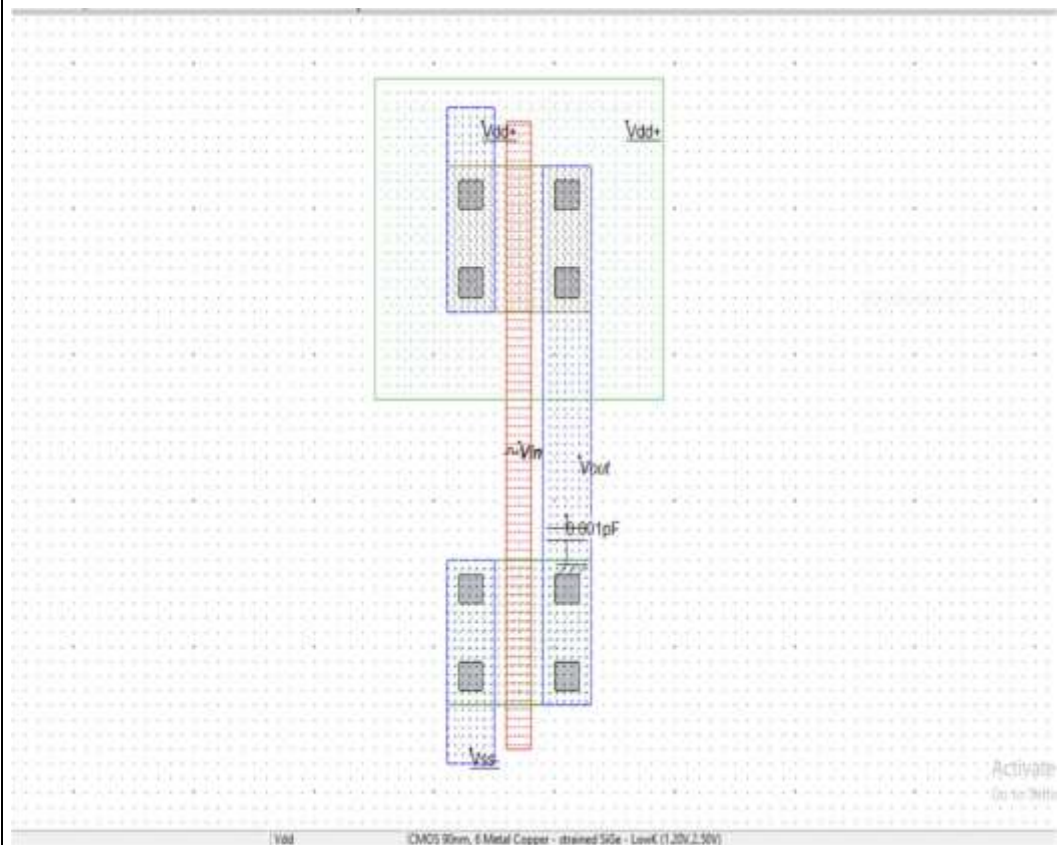


Waveforms:

 
1: $CL=0.001\text{pF}$ and $F=5\text{GHz}$



 
2: $CL=0.002\text{pF}$ and $F=5\text{GHz}$



 3: $CL=0.0005\text{pF}$ and $F=5\text{Ghz}$



 4: $CL=0.001\text{pF}$ and $F=10\text{Ghz}$




5: $CL=0.001\text{pF}$ and $F=2.5\text{Ghz}$



SR.NO	C_{load} (pF)	Value (uW)
1)	0.001	12.488
2)	0.002	18.627
3)	0.0005	9.485

SR.NO	f_{clk} (GHz)	Value (uW)
1)	5	12.488
2)	2.5	6.712
3)	10	23.834

Layout for 180nm foundry:

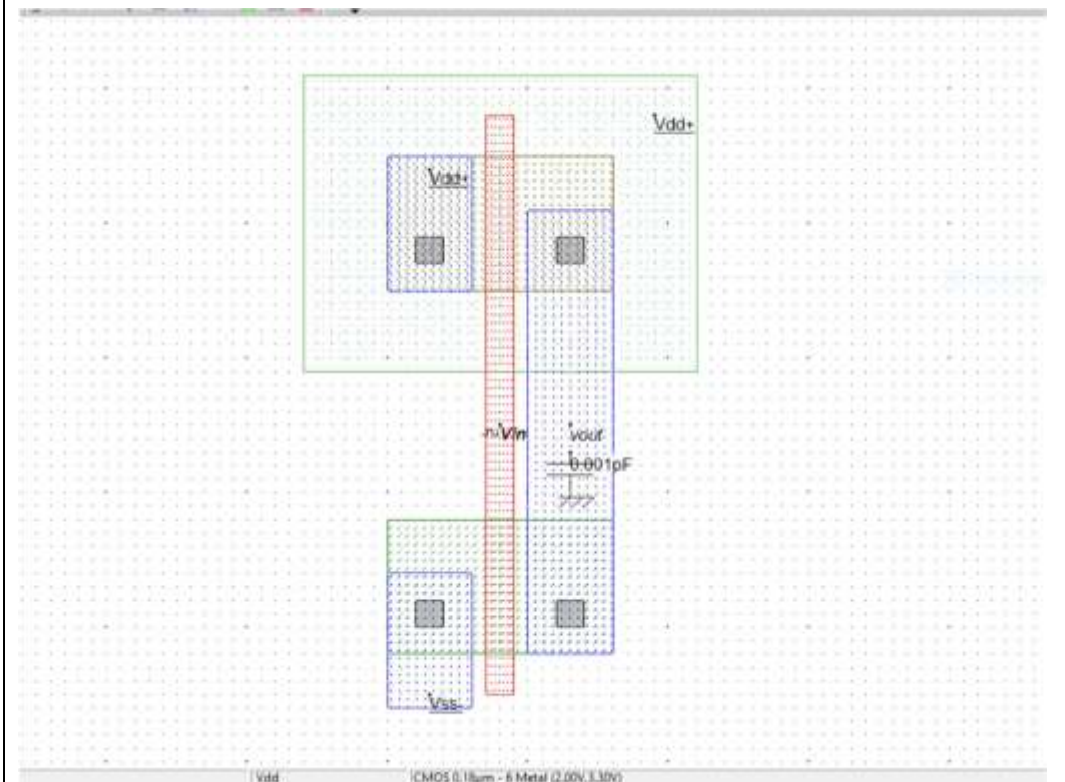

Waveforms:-



Pdynamic Analysis: $V_{dd} = 2 \text{ V}$

Sr.No	C_{load} (pF)	f_{clk} (GHz)	$P_{dynamic}$
1	0.001	5 GHz	40.32 μW

Conclusion:-

Thus we have :

- 1) Drawn the LAYOUT for CMOS Inverter using 90 nm & 180 nm Foundry.
- 2) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-TABLE.
- 3) Noted the values of $P_{dynamic}$ for floating Load.
- 4) Appreciated the validity of the mathematical model :
$$P_{dynamic} = C_L * (V_{dd})^2 * f_{clk}$$
 by Doubling & Halving the values of C_L & f_{clk}
- 5) Found a reduction in $P_{dynamic}$ by using a better Foundry i.e., 90 nm instead of 180 nm

Class	BE-6
Roll Number	42247
Assignment Number	B.1.b
Assignment Name	NAND-AND , NOR-OR Gates
Date of performance	06/10/2021

SYMBOLS:-

2 i/p OR Gate



$$Y_{or} = A + B$$

2 i/p NAND Gate




$$Y_{\text{nand}} = \overline{A \cdot B}$$

2 i/p AND Gate



$$Y_{\text{and}} = A \cdot B$$


2 i/p NOR Gate

 


$$Y_{\text{nand}} = \overline{A + B}$$

MOSFET-LEVEL SCHEMATICS :

NAND- AND Gate

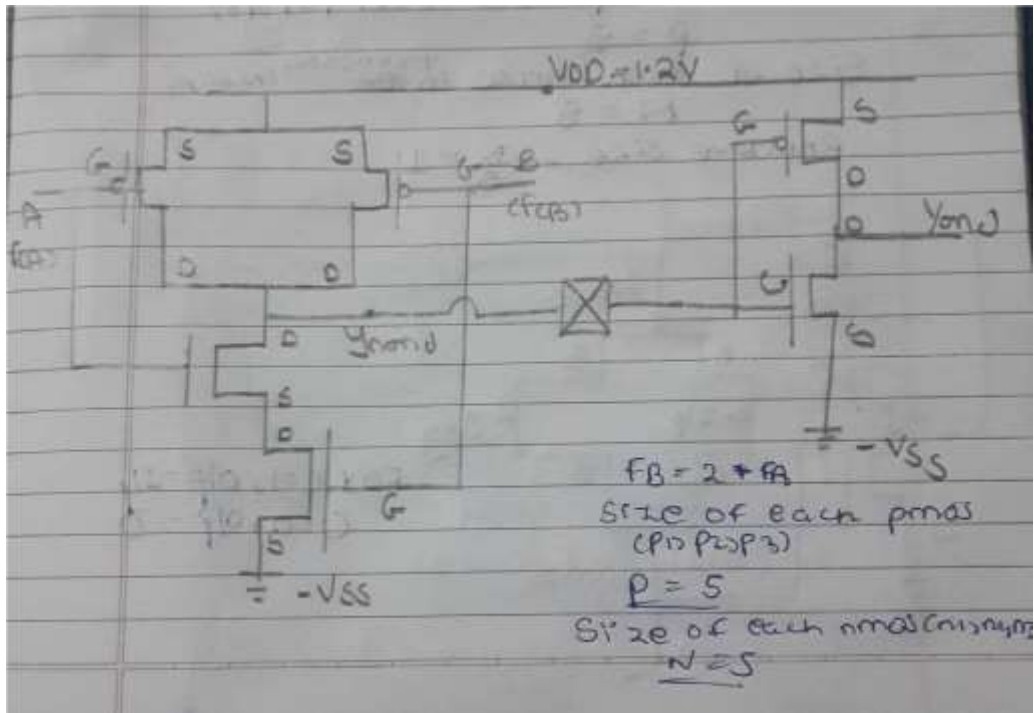

NOR-OR Gate

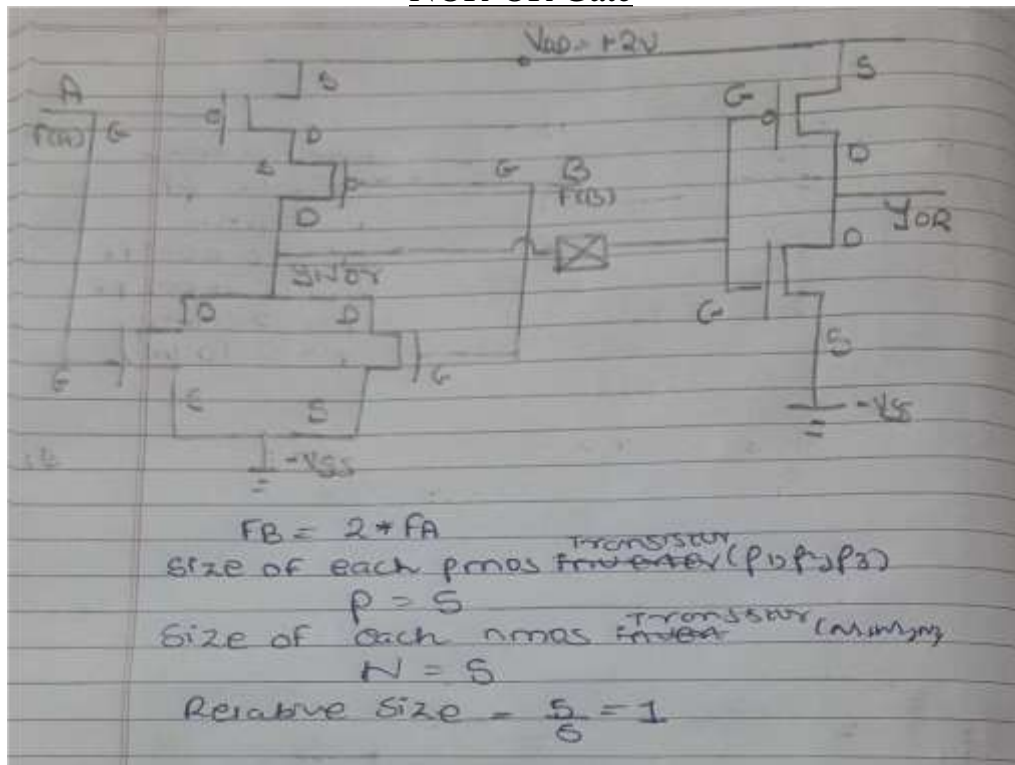

Truth Table:-

1. Nand Gate

A	B	Y _{nand}
0	0	1
0	1	1
1	0	1
1	1	0

2. And Gate

A	B	Y _{and}
0	0	0
0	1	0
1	0	0
1	1	1

3.Nor Gate


A	B	Ynor
0	0	1
0	1	0
1	0	0
1	1	0

4. Or Gate

A	B	Yor
0	0	0
0	1	1
1	0	1
1	1	1


Layouts:

1.NAND Gate

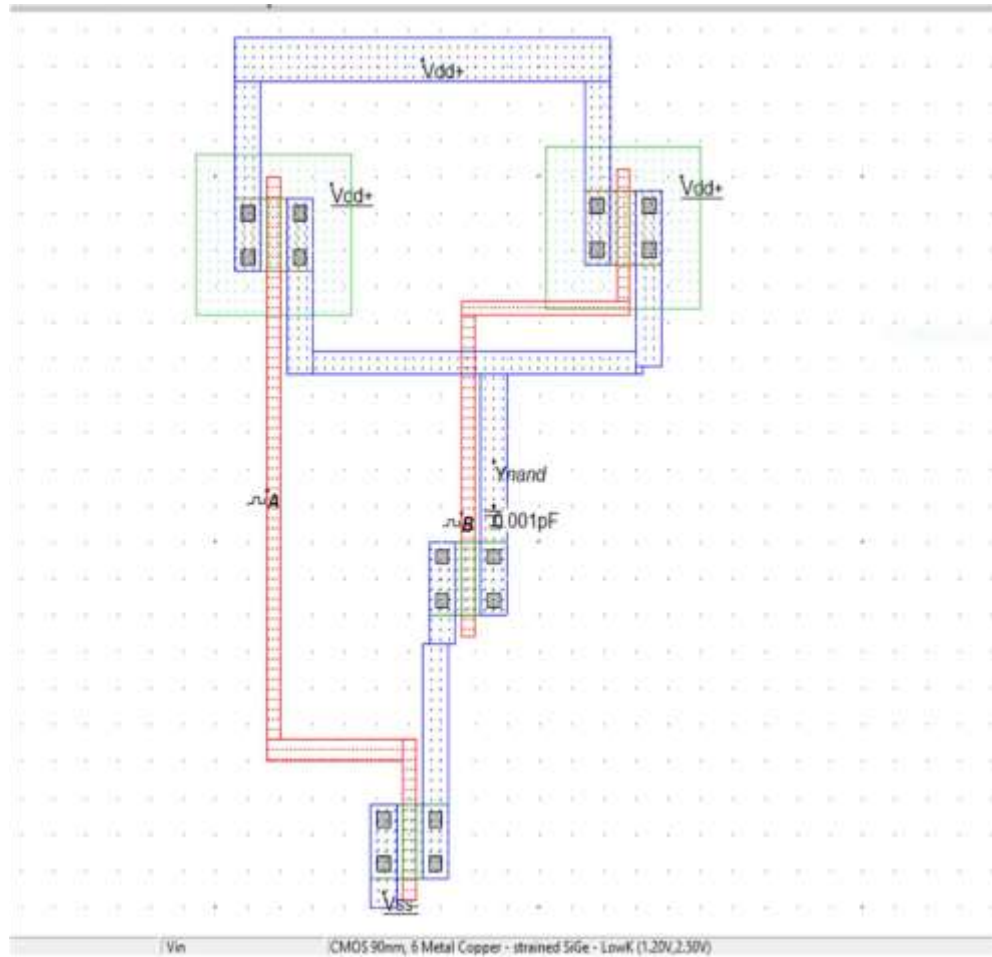


2.

AND Gate

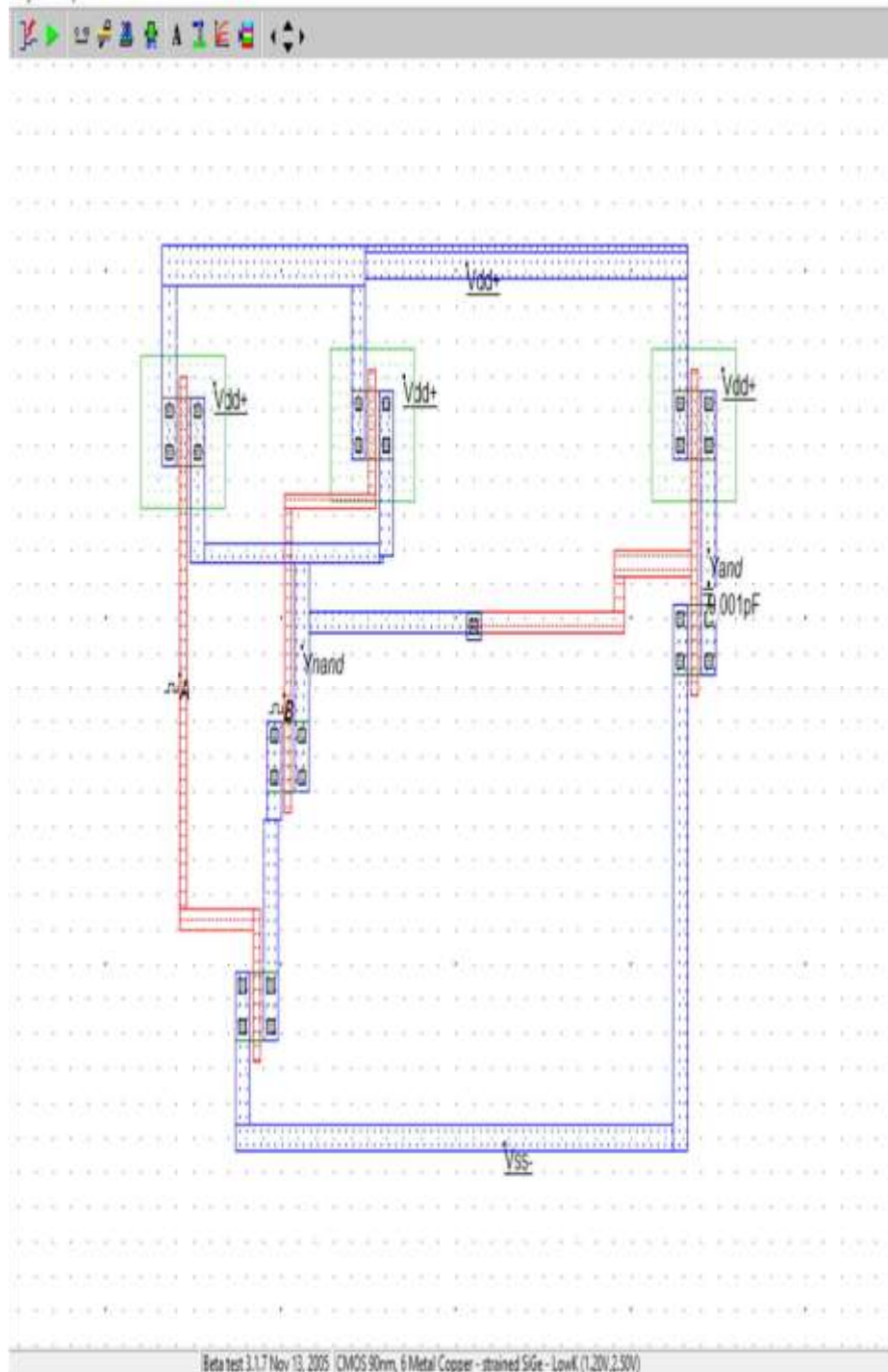

3.


NOR Gate

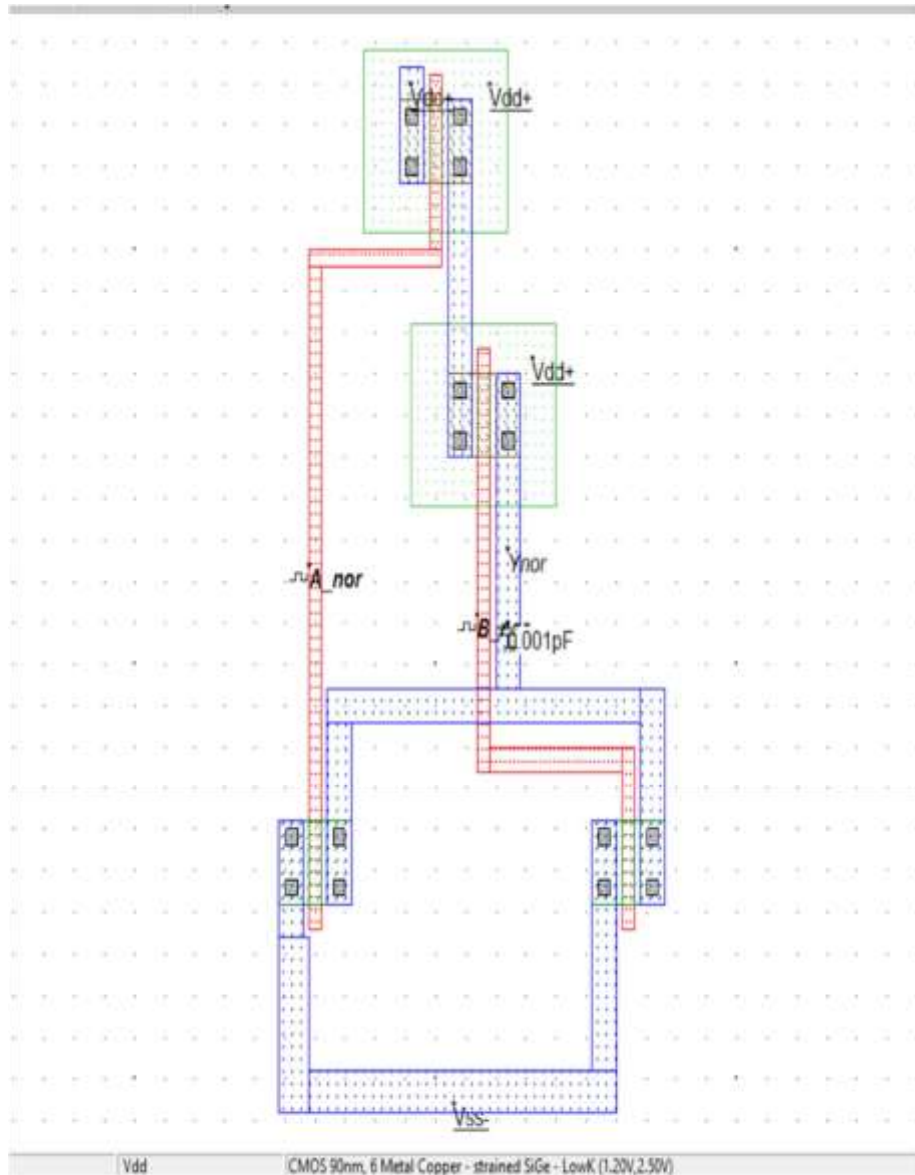

4.


OR Gate

5.

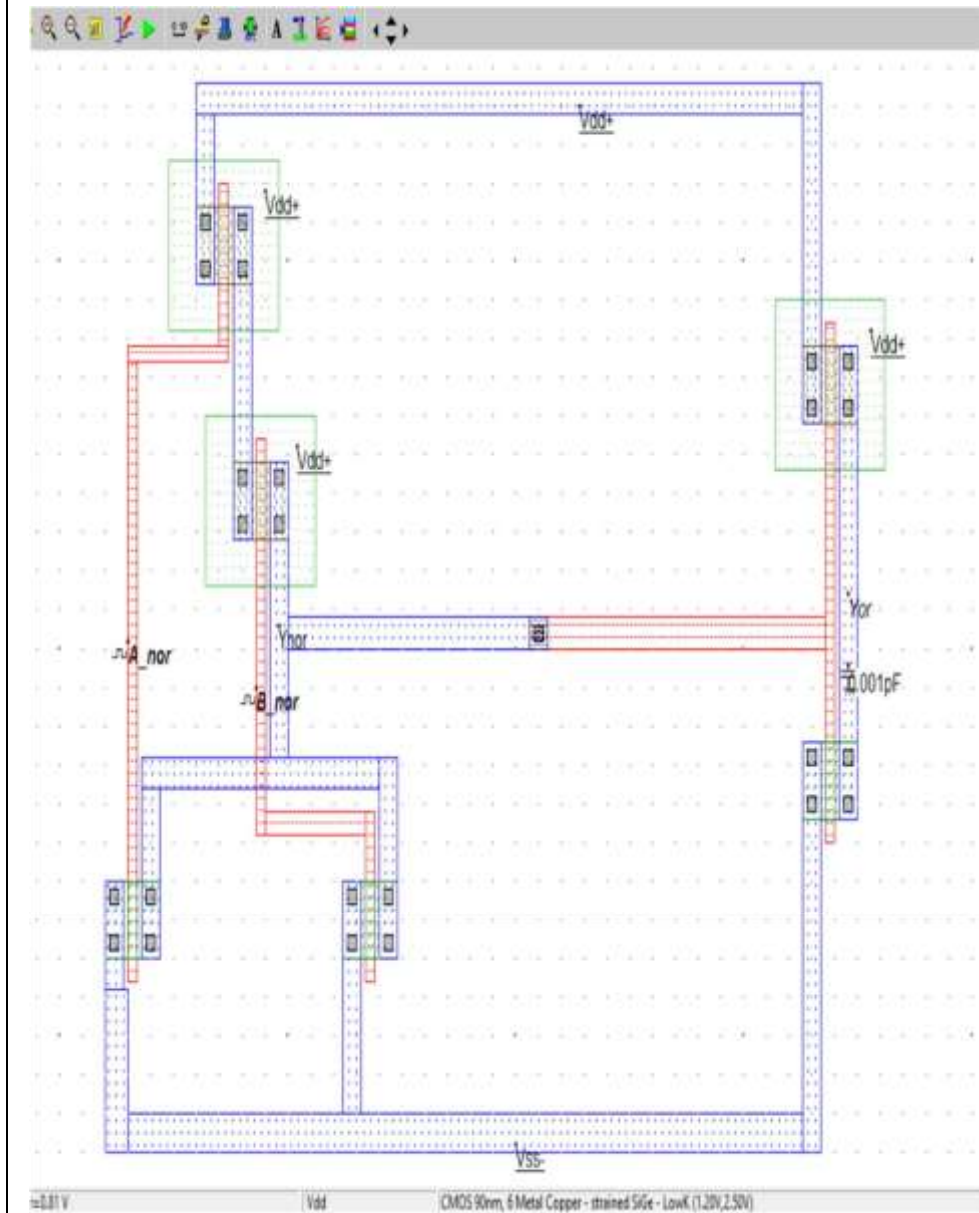


Waveforms :


1. NAND Gate

 


2. AND Gate

 

3. NOR Gate

 

4. OR Gate

 

Conclusion:-

Thus we have :


-
- 1) Drawn the LAYOUT for CMOS NAND-AND , NOR-OR Gates using 90 nm Foundry.

2) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-


TABLE.

Class	BE-6
Roll Number	42247
Assignment Number	B.1.c
Assignment Name	Transmission Gate
Date of performance	27/10/2021

Block Diagram:-

 

MOSFET-LEVEL SCHEMATIC :

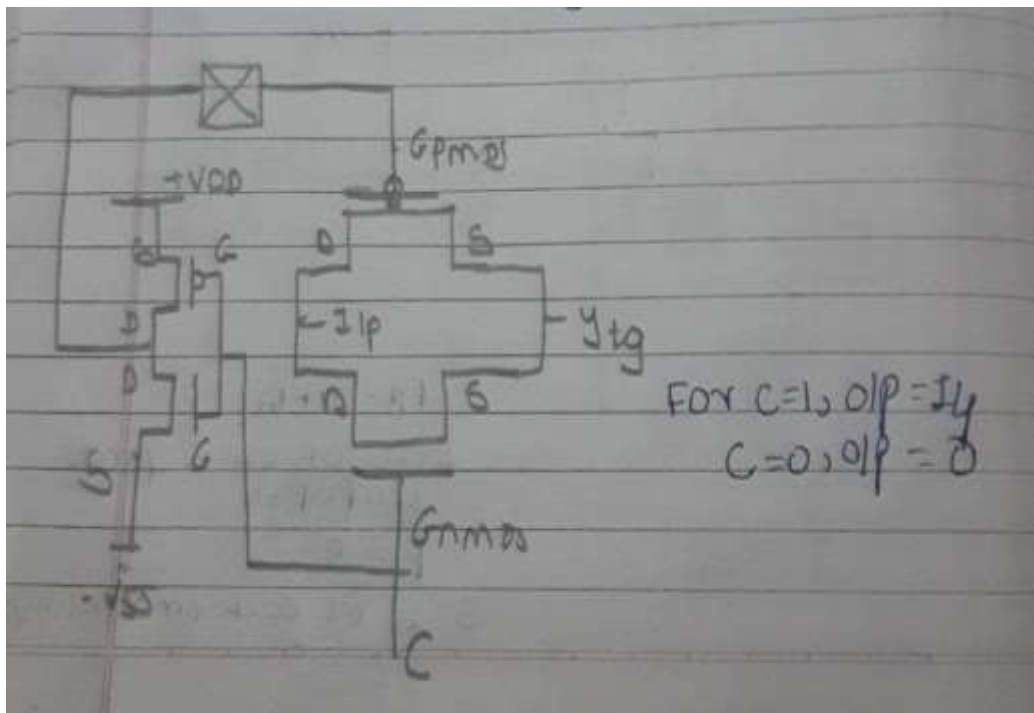


Truth Table:-

C	Y_{lg}
1	Input=1 / 0 , Strong -1 / Strong -0
0	I/P = Don't Care


Layout:

1. TG layout:

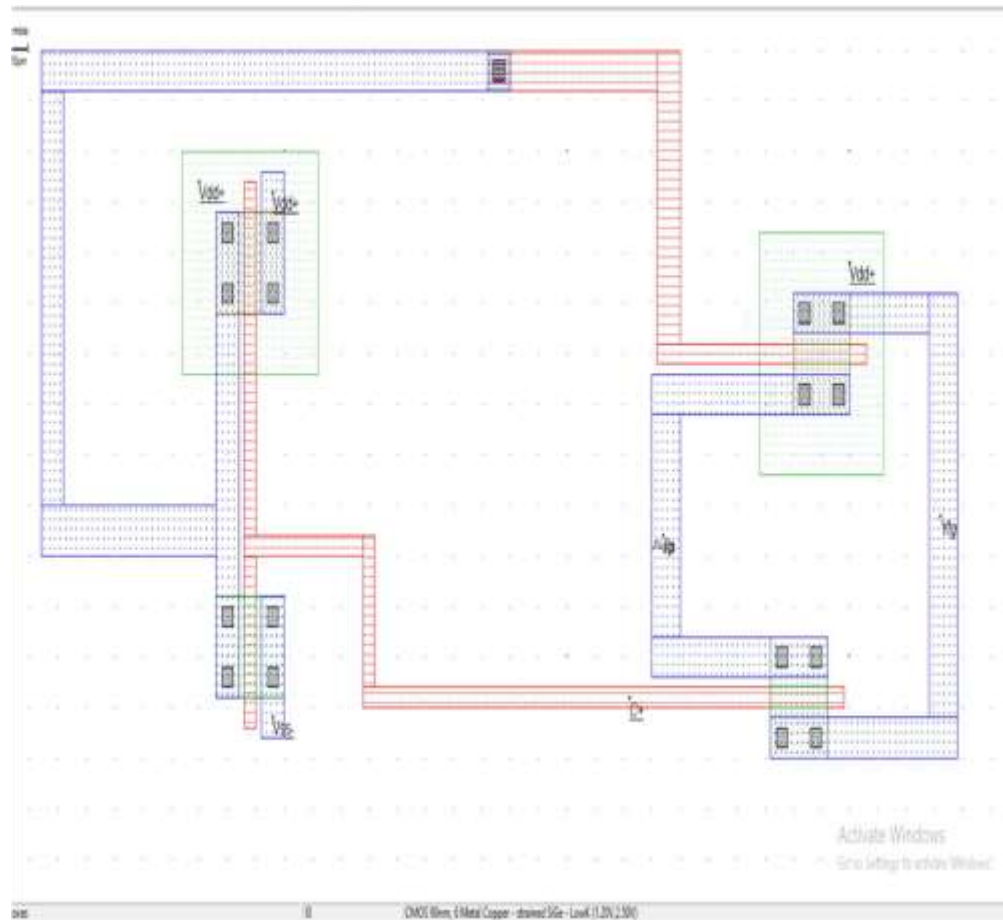


Waveform:

1: TG with C=1

 

Y_{tg} follows I/P , $Y_{tg} = \text{Strong-1} / \text{Strong-0}$ for I/P = 1 / 0

2: TG with C=0

 

Y_{tg} does not follows I/P

Conclusion:-


Thus we have :

-
- 1) Drawn the LAYOUT for TRANSMISSION GATE using 90 nm Foundry.
 - 2) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-TABLE.


3) TG gives STRONG-1 ,STRONG-0 for I/P = 1 / 0 Respectively.


Class	BE-6
Roll Number	42247
Assignment Number	B.1.d
Assignment Name	Half-Adder Using MUX Using TG
Date of performance	27/10/2021


Block Diagrams:-

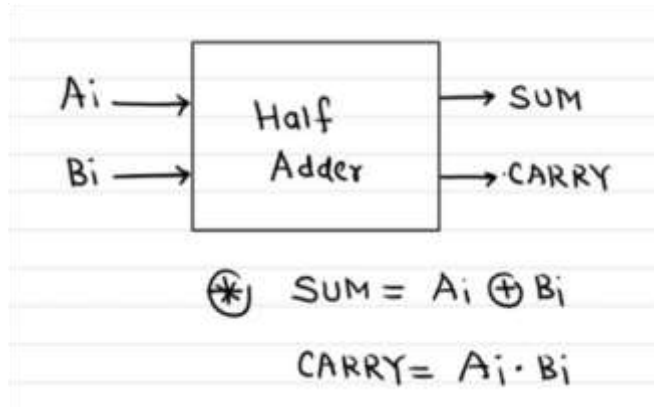


Gate-Level Schematic:-

 

 

 


BLOCK-LEVEL SCHEMATIC :

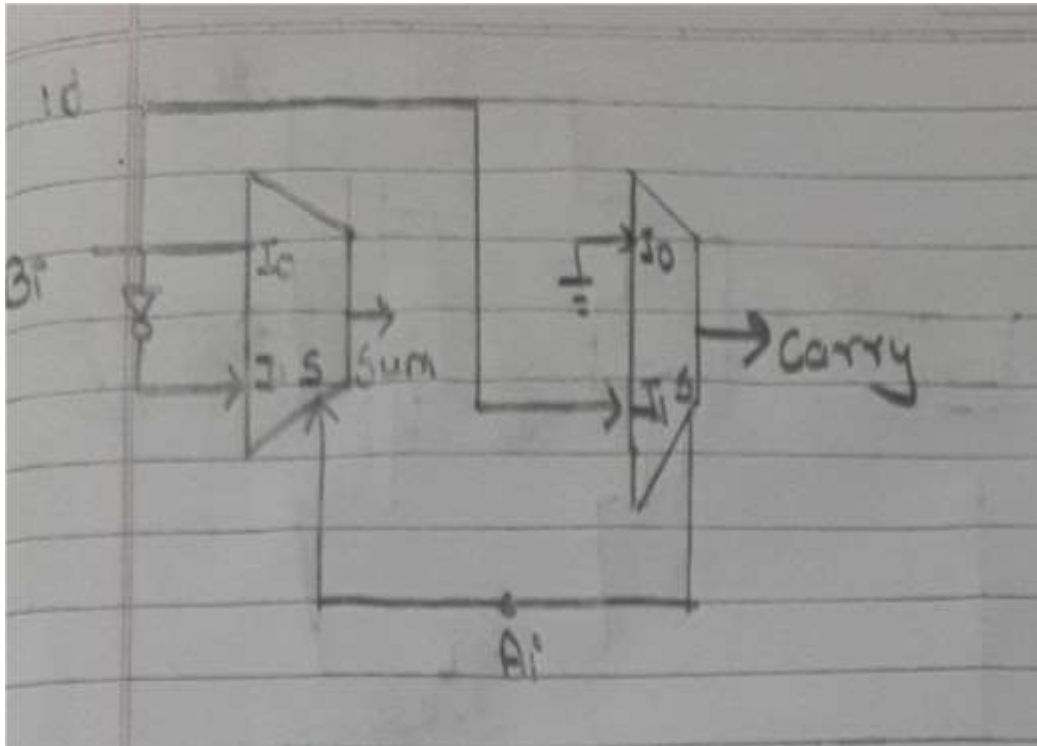


Truth Table:-

Ai	Bi	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Layouts:

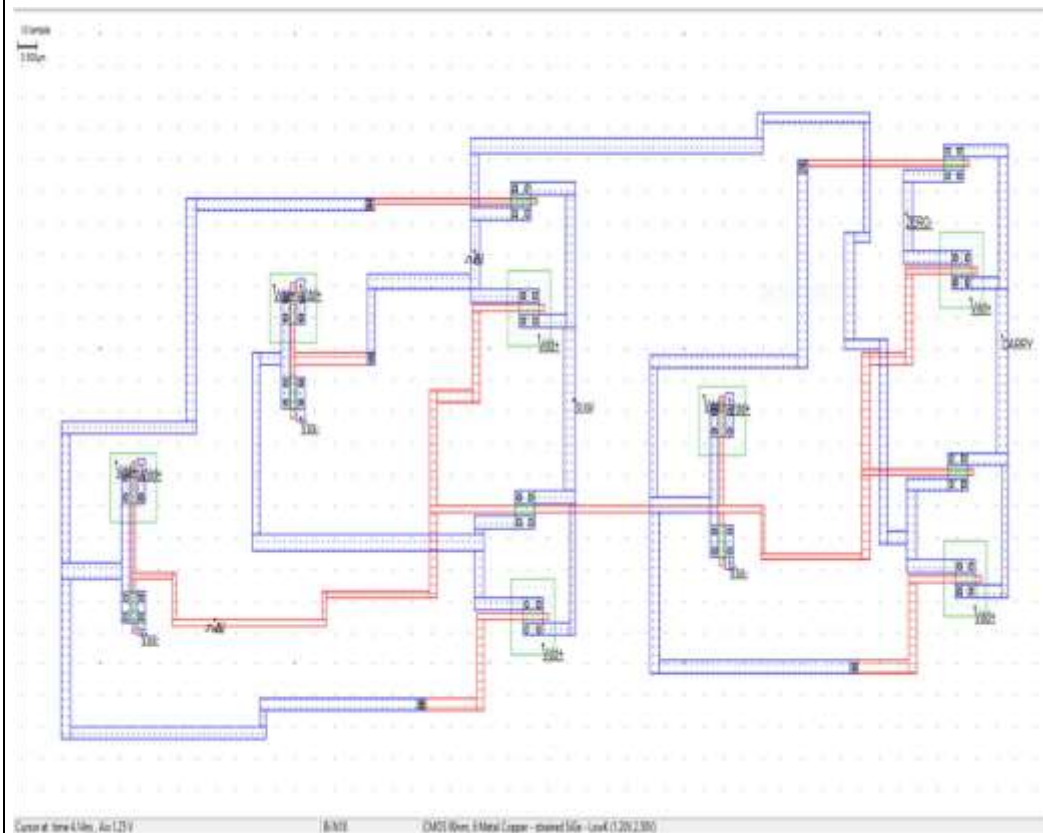

Waveform:

 

Conclusion:-

Thus, we have :


- 1) Drawn the LAYOUT for HALF-ADDER using 90 nm Foundry.
- 2) HALF-ADDER is implemented as a combination of EX-OR Gate & AND Gate.
- 3) EX_OR Gate & AND Gate are Implemented as a Modification of TWO 2:1 MUX's.
- 4) Each MUX is implemented as a combination of 2 TG's.

5) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-

TABLE.

Class	BE-6
Roll Number	42247
Assignment Number	B.2
Assignment Name	2:1 Mux using Transmission Gate
Date of performance	13/10/2021


Block Diagram:-

 


Truth Table:-

S	Ymux
0	I0
1	I1


MOSFET-LEVEL SCHEMATIC :-

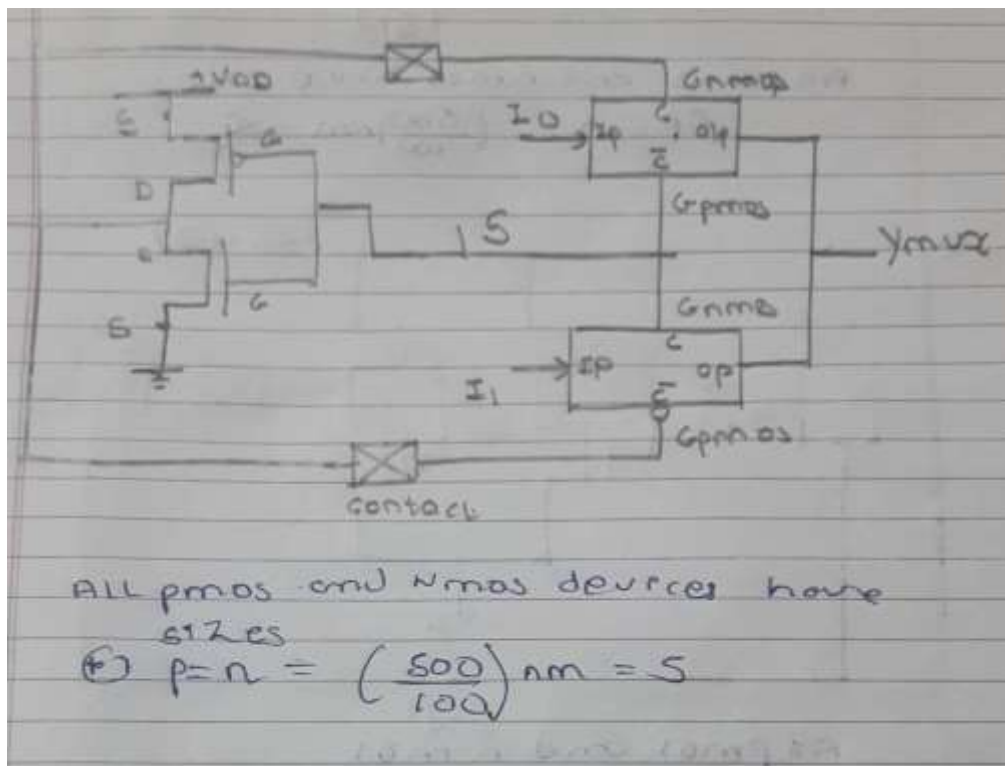

Layout:

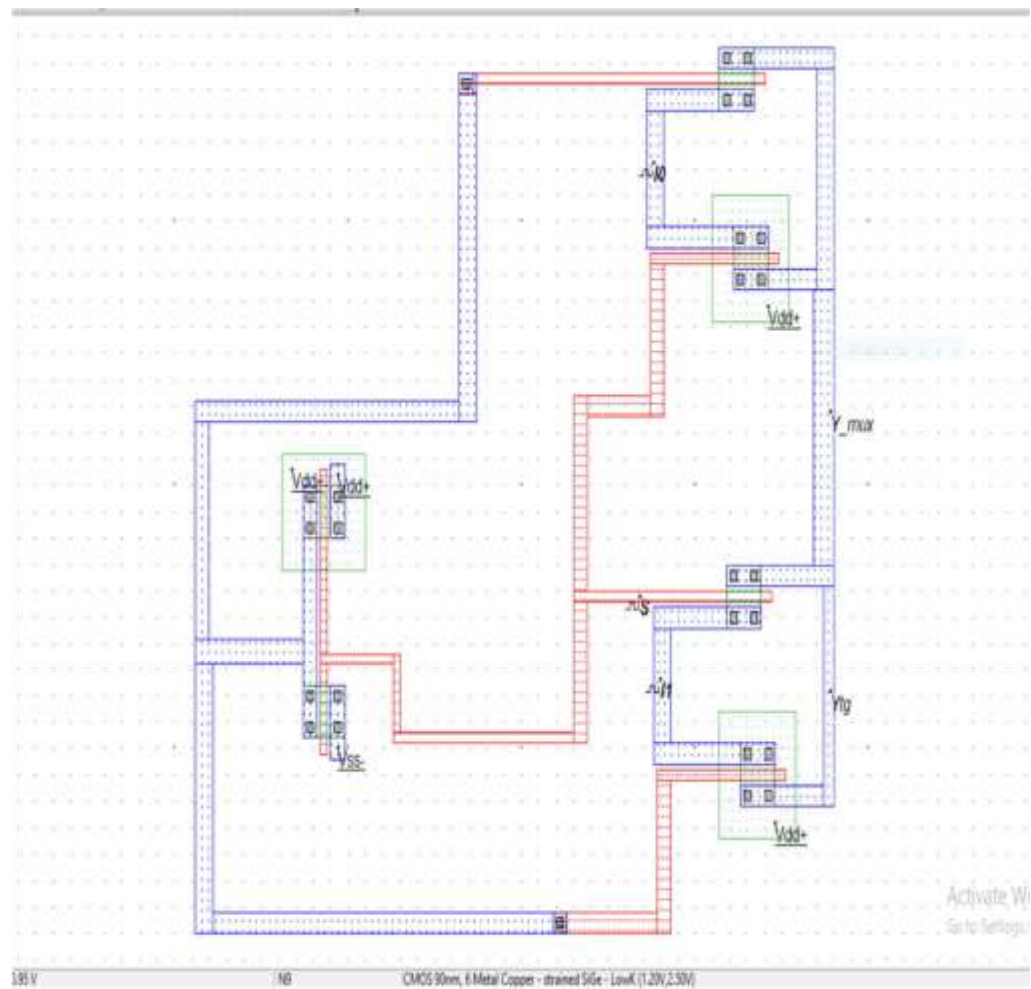

Waveform:

 


Conclusion:-

Thus we have :

- 1) Drawn the LAYOUT for 2:1 MUX using 90 nm Foundry.
- 2) MUX is implemented as a combination of 2 Transmission Gates.
- 3) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-TABLE.

Class	BE-6
Roll Number	42247
Assignment Number	B.3.a
Assignment Name	1-bit SRAM cell using NMOS Switches
Date of performance	10/11/2021


MOSFET-LEVEL SCHEMATIC :-

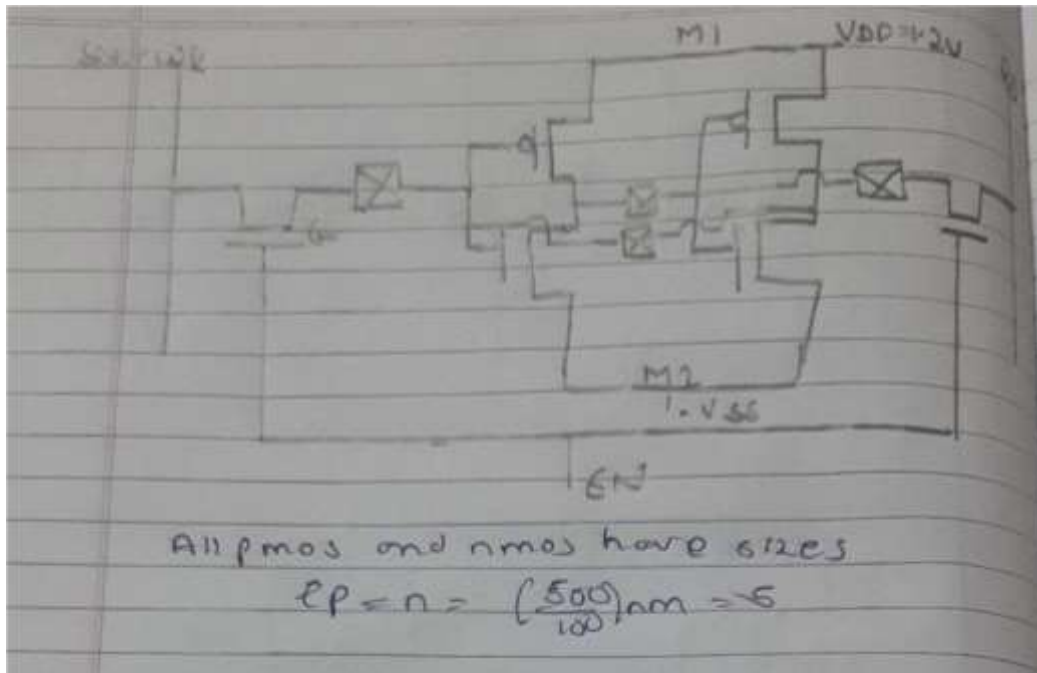

Truth Table:-


C	WR	RD
1	0	Weak-1
1	1	Strong-0
0	X	0/Hold

Layout:

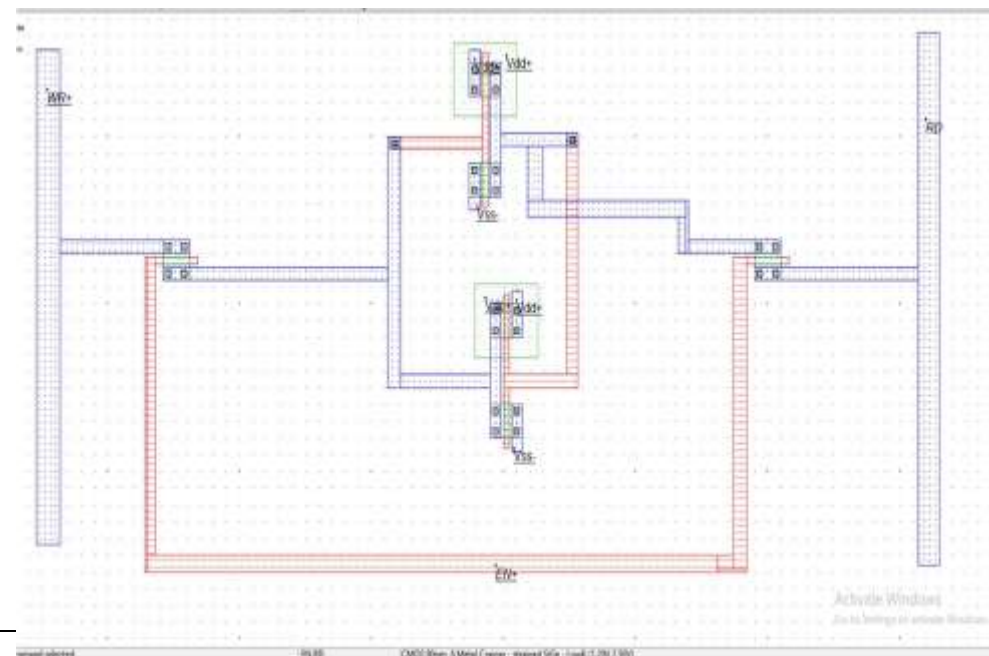

Waveform:

1: $C=1$, $WR=0$, $RD = \text{Weak-1}$:

 

2: $C=1$, $WR=1$, $RD = \text{Strong-0}$:



3: C=0, WR = 0, RD= HOLD




Conclusion:-

Thus we have :

- 1) Drawn the LAYOUT for 1-bit SRAM Cell Using NMOS Switches using 90 nm Foundry.
- 2) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-TABLE.
- 3) Logic-0 gets written as WEAK-1 (Unacceptable)
- 4) Logic-1 gets written as STRONG-0 (Acceptable)

Class	BE-6
Roll Number	42247
Assignment Number	B.3.b
Assignment Name	1-bit SRAM cell using Transmission Gate Switches
Date of performance	10/11/2021


MOSFET-LEVEL SCHEMATIC :-

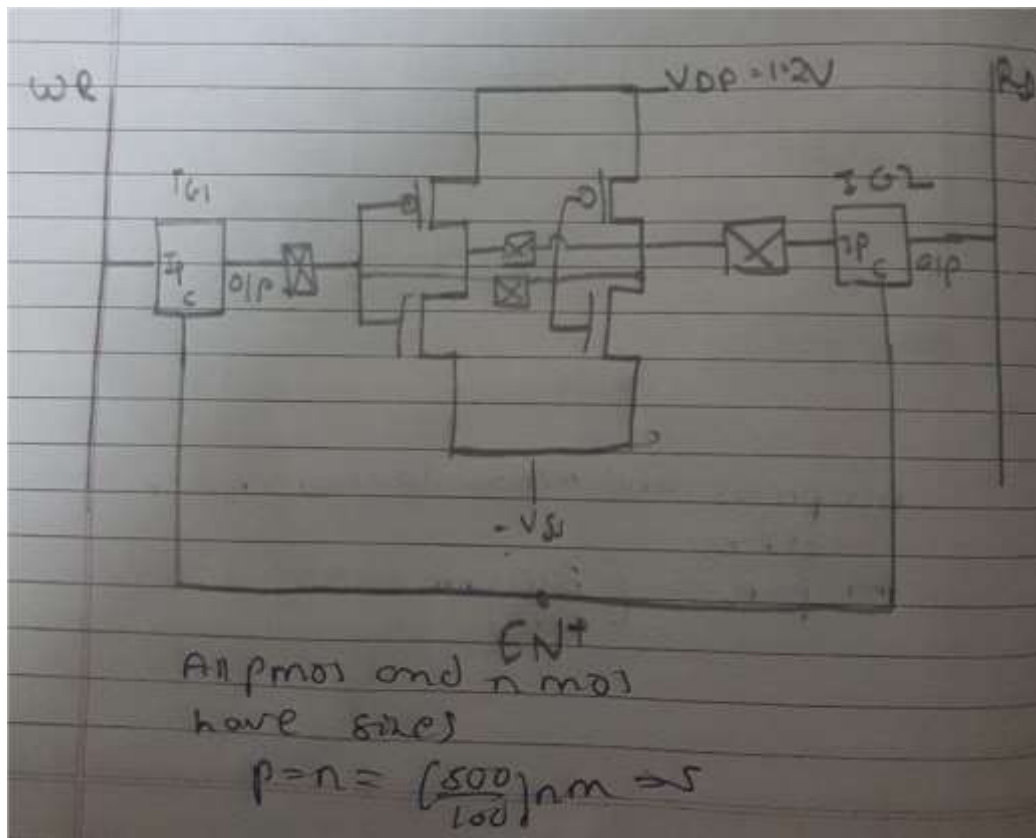

Truth Table:-


C	WR	RD
1	0	Strong-1
1	1	Strong-0
0	X	0/Hold

Layout:

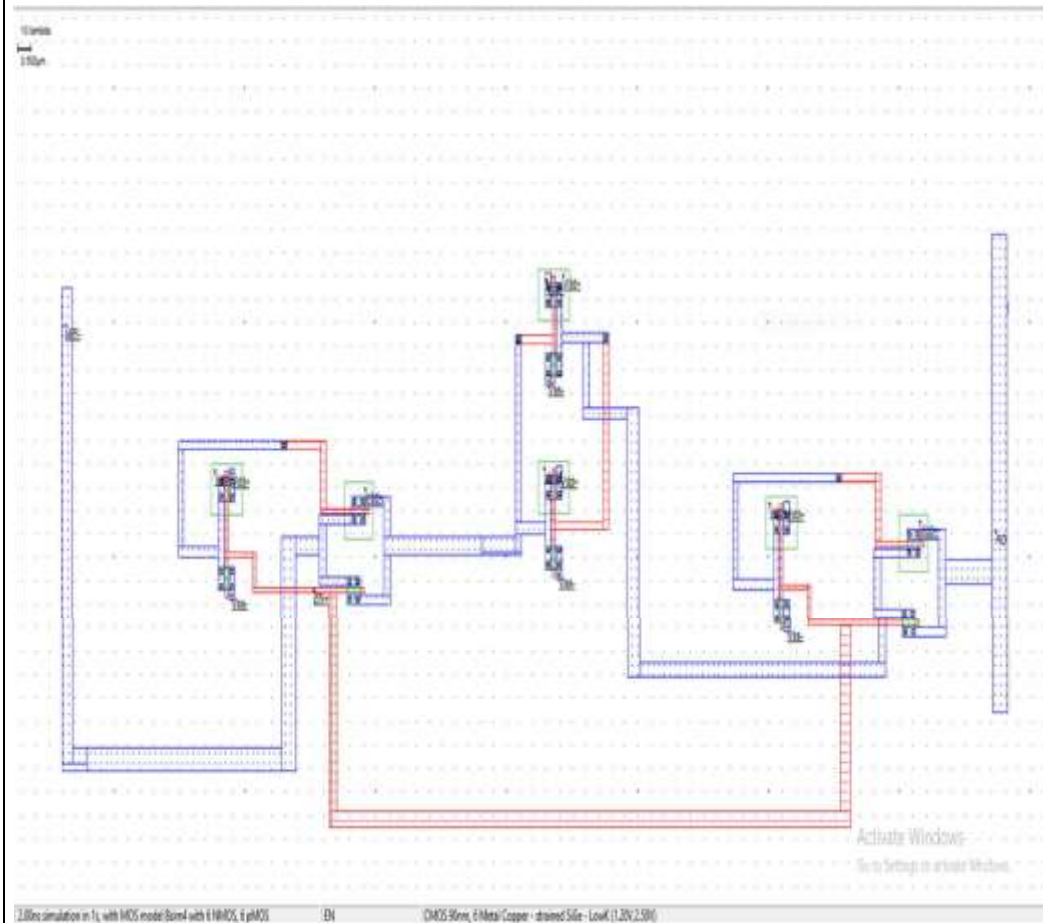

Waveforms:

 1: $C=1, WR = 0$, $RD = \text{Strong-1}$:



2: $C=1, WR=1, RD = \text{Strong-0}$



3: C=0, WR=0, RD = 0



Conclusion:-

Thus we have :

- 1) Drawn the LAYOUT for I-bit SRAM Cell Using TG Switches using 90 nm Foundry.
- 2) Simulated the LAYOUT to observe waveforms & verified its functionality as per TRUTH-TABLE.
- 3) Logic-0 gets written as STRONG-1 (Acceptable)
- 4) Logic-1 gets written as STRONG-0 (Acceptable)
